

Integer Multiplier

ECE-111 Advanced Digital Design Project

Vishal Karna


Homework-6b : Integer Multiplier

□ Develop SystemVerilog RTL model for N-bit Integer Multiplier

- Develop Finite state machine and state transition diagram for SHIFT and ADD multiplier algorithm
- FSM coding style recommended : Single always block with non-blocking assignment statements within always block.
- Synthesize integer multiplier design for parameter N=4 and run simulation using testbench provided
- Review synthesis results (resource usage and RTL netlist/schematic)
- Review input and output signals in simulation waveform.
- Assume below mentioned primary port names and SystemVerilog RTL module **integer_multiplier**.
- **FSM code framework is provided in Lab folder with comments to help develop the code.**
- **Integer Multiplier testbench provided in Lab folder has built in checker to ensure design output is expected. See messages in Modelsim transcript window when performing simulation**

□ Primary Ports for integer_multiplier module

- **Input** clock, reset : asynchronous posedge reset
- **Input** start : 1 cycle pulse generated. Indicates to FSM to start multiplication operation
- **Input** logic[N-1:0] multiplicand, multiplier : Multiplicand and Multiplier inputs to Integer Multiplier
- **Output** logic[(2*N):0] product : Result of multiplication includes carry bit as MSB bit
- **Output** logic done : indicates that product is available. This is one cycle pulse generated by FSM

 


Homework-6b : Integer Multiplier

□ Report should include :

- SystemVerilog FSM design code, State transition diagram (hand drawn snapshot or Snapshot from Quartus either way is fine) and Quartus auto-generated State transition table.
- Synthesis resource usage and schematic generated from RTL netlist viewer
- Simulation snapshot, simulation results transcript snapshot and explain simulation result to confirm RTL model developed works as a integer multiplier

□ Reference Output Snapshot

 

SHIFT And ADD Method to Perform Integer Multiplier

- ❑ Multiplier : 4'b1101 (13), Multiplicand : 4'b1011 (11), Expected Product = 11 x 13 = 143 (9'b0_1000_0111)
- ❑ N-bit Multiplier has N stages of SHIFT and ADD round of computation
- ❑ If Multiplier LSB[0] = 1 Perform ADD of Accumulator + Multiplicand and store back to Accumulator and then perform Right Shift by 1
- ❑ If Multiplier LSB[0] = 0 Perform Right Shift by 1

	Stage-1	Carry	Accumulator	Multiplier	Operation Performed
acc + multiplicand 0 0 0 0 + 1011 = 01011	0	0	0 0 0 0	1 1 0 1	Initialize
	1	0	1 0 1 1	1 1 0 1	ADD
		0	0 1 0 1	1 1 1 0	SHIFT >> 1
acc + multiplicand 0 0 1 0 + 1011 = 01101	2	0	0 0 1 0	1 1 1 1	SHIFT
	3	0	1 1 0 1	1 1 1 1	ADD
		0	0 1 1 0	1 1 1 1	SHIFT >> 1
acc + multiplicand 011 0 + 1011 = 1000	4	1	0 0 0 0	1 1 1 1	ADD
		0	1 0 0 0	0 1 1 1	SHIFT >> 1


SHIFT And ADD Integer Multiplier Algorithm Summary

❑ Multiplication Process and FSM States :

- **IDLE:** Wait in this state until Start=1. Then move to INITIALIZE state if input signal Start==1
- **INITIALIZE:** Multiplicand and multiplier are loaded into a load register and a shift register, respectively;
- **TEST:** The LSB in the shift register which contains the multiplier is tested to decide the next state. If shift register LSB is '1', then next state is to **ADD** otherwise next state is to **SHIFT_AND_COUNT**
- **ADD:** the Adder adds previous stage add result with Multiplicand and stores the product to the accumulation result, back to shift register and then the state machine transits to **SHIFT_AND_COUNT** state
- **SHIFT_AND_COUNT:** If shift register content is right shifted by 1 bit position. MSB of shift register '0' is entered
- When the counter reaches to N, then next state is **DONE** stage otherwise next state is **TEST** state for next stage ADD/SHIFT operation
- **DONE:** Done signal is asserted to '1' and shift register content is sent to 'product' output signal

Homework Assignment : Integer Multiplier

 
- ❑ Quartus Generated State Machine Diagram and State Table for reference purpose




	Source State	Destination State	Condition
1	ADD	SHIFT_AND_COUNT	
2	DONE	IDLE	
3	IDLE	IDLE	(!start)
4	IDLE	INITIALIZE	(start)
5	INITIALIZE	TEST	
6	SHIFT_AND_COUNT	TEST	(!count[0]) + (count[0]).(!count[1])
7	SHIFT_AND_COUNT	DONE	(count[0]).(count[1])
8	TEST	SHIFT_AND_COUNT	(!shift_reg[0])
9	TEST	ADD	(shift_reg[0])

Note : When FSM transition to DONE state, load "shift_reg" value to "product"
And set done = 1 from separate logic using assign statement

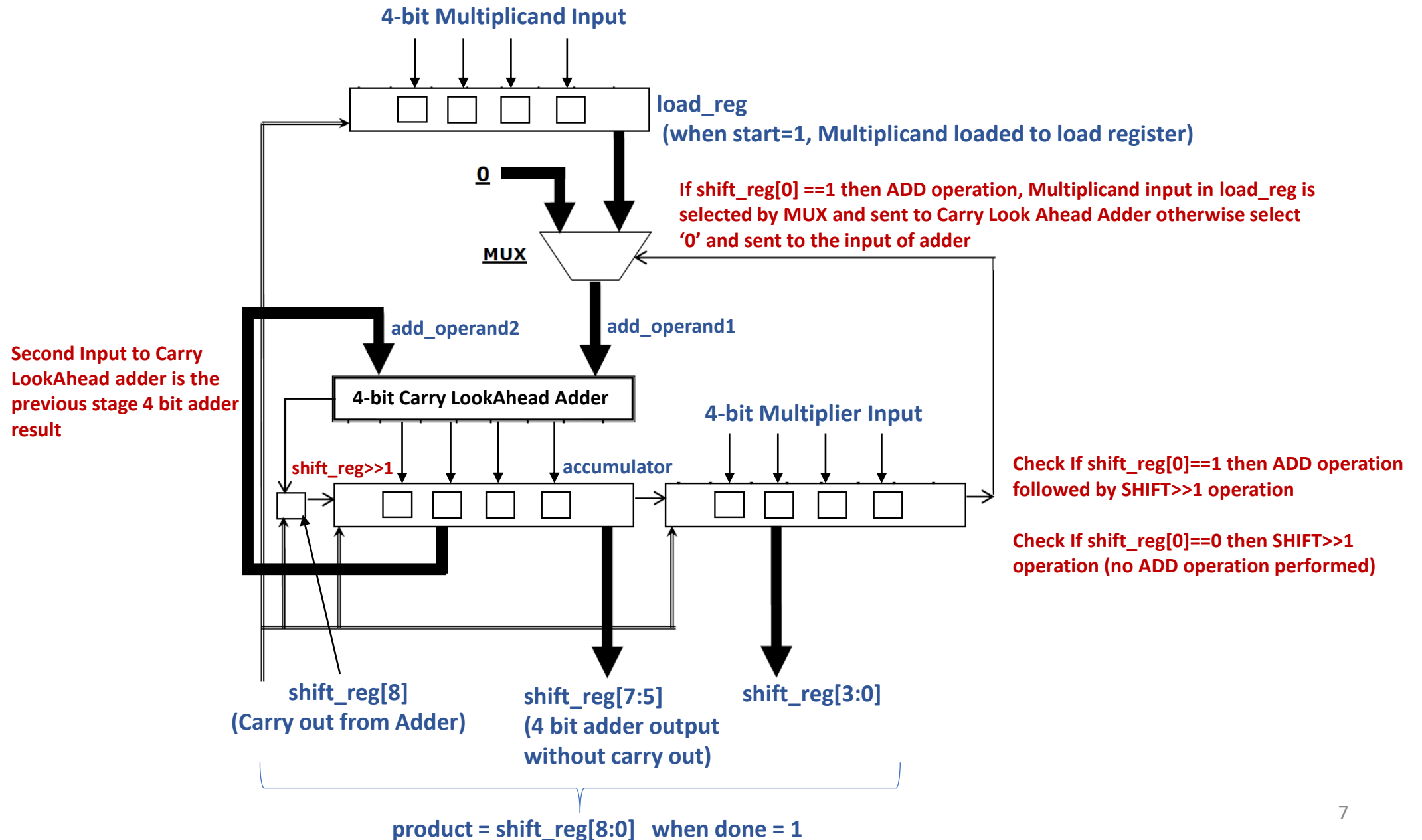Block Diagram of Integer Multiplier Using SHIFT and ADD



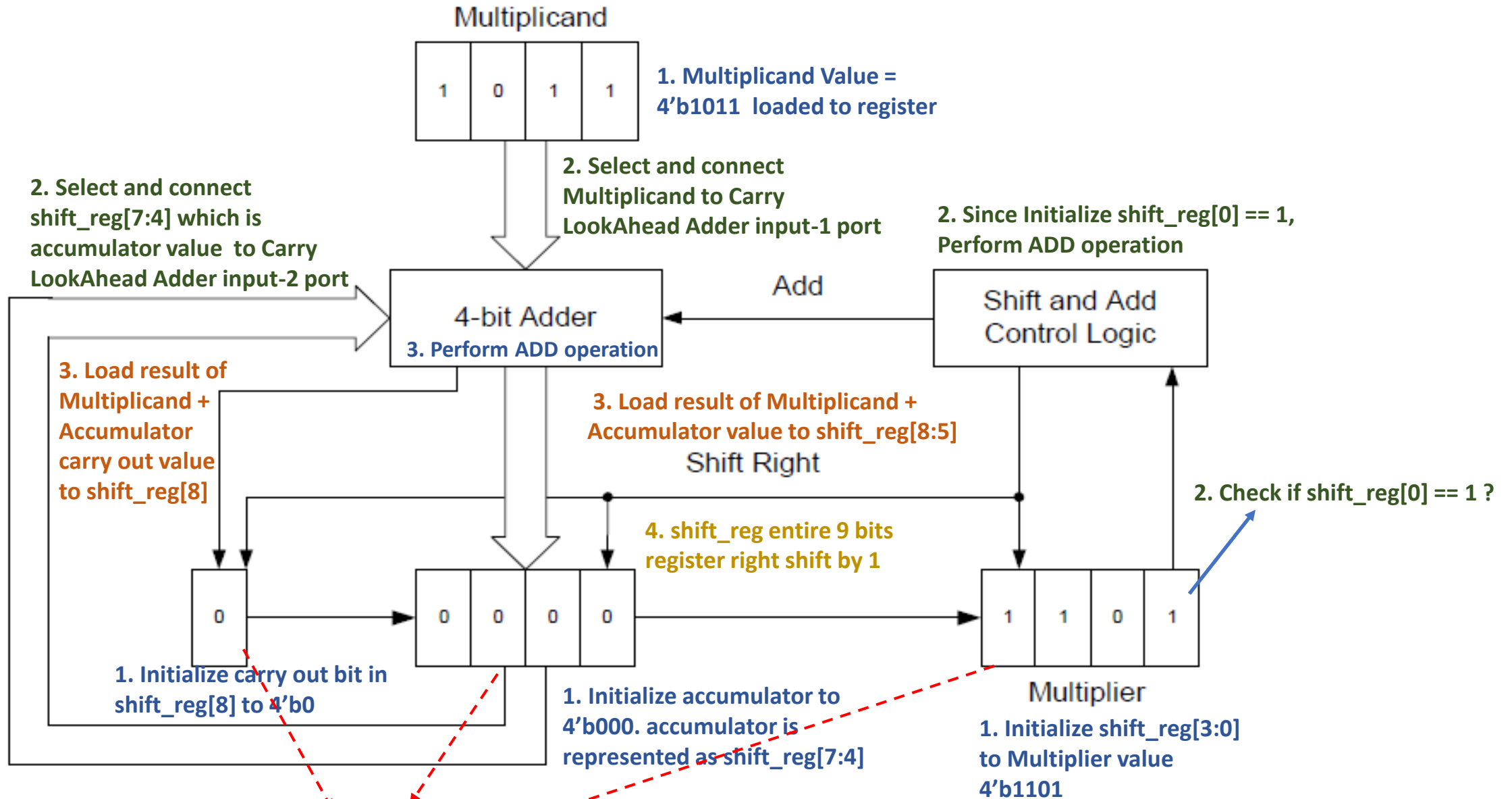SHIFT And ADD Integer Multiplier Algorithm Steps Summary




At end of stage-0 count, shift_reg = {0, 4'b0101, 4'b1110}, Repeat these steps until count value == N. And end of stage-3 count, final product will be available

**Let's us do simulation of 4-bit Integer Multiplier
using SHIFT and ADD Multiplier Algorithm**


SHIFT And ADD Integer Multiplier Algorithm Example Steps

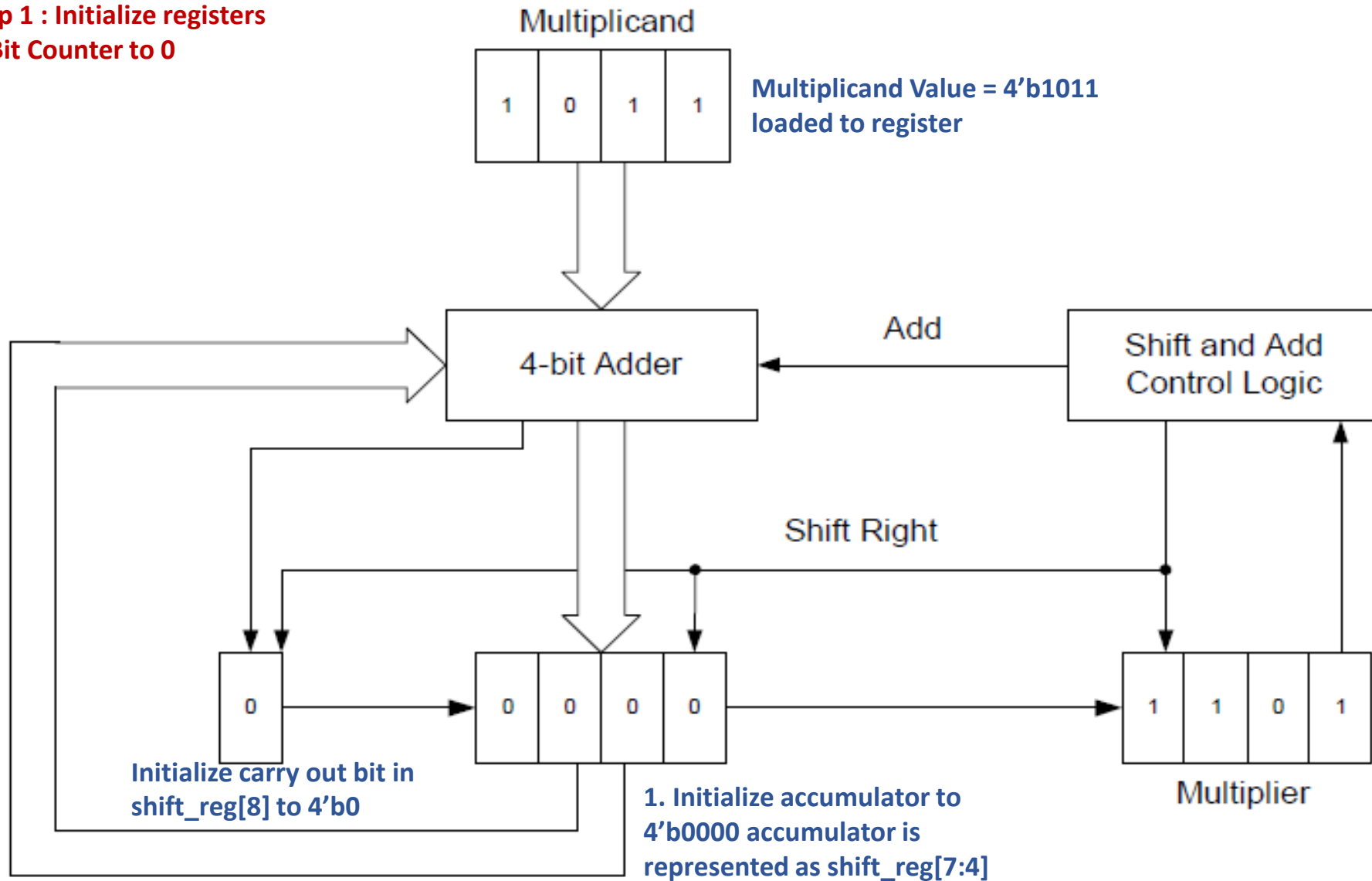Step 1 : Initialize registers
N-Bit Counter to 0



SHIFT And ADD Integer Multiplier Algorithm Example Steps

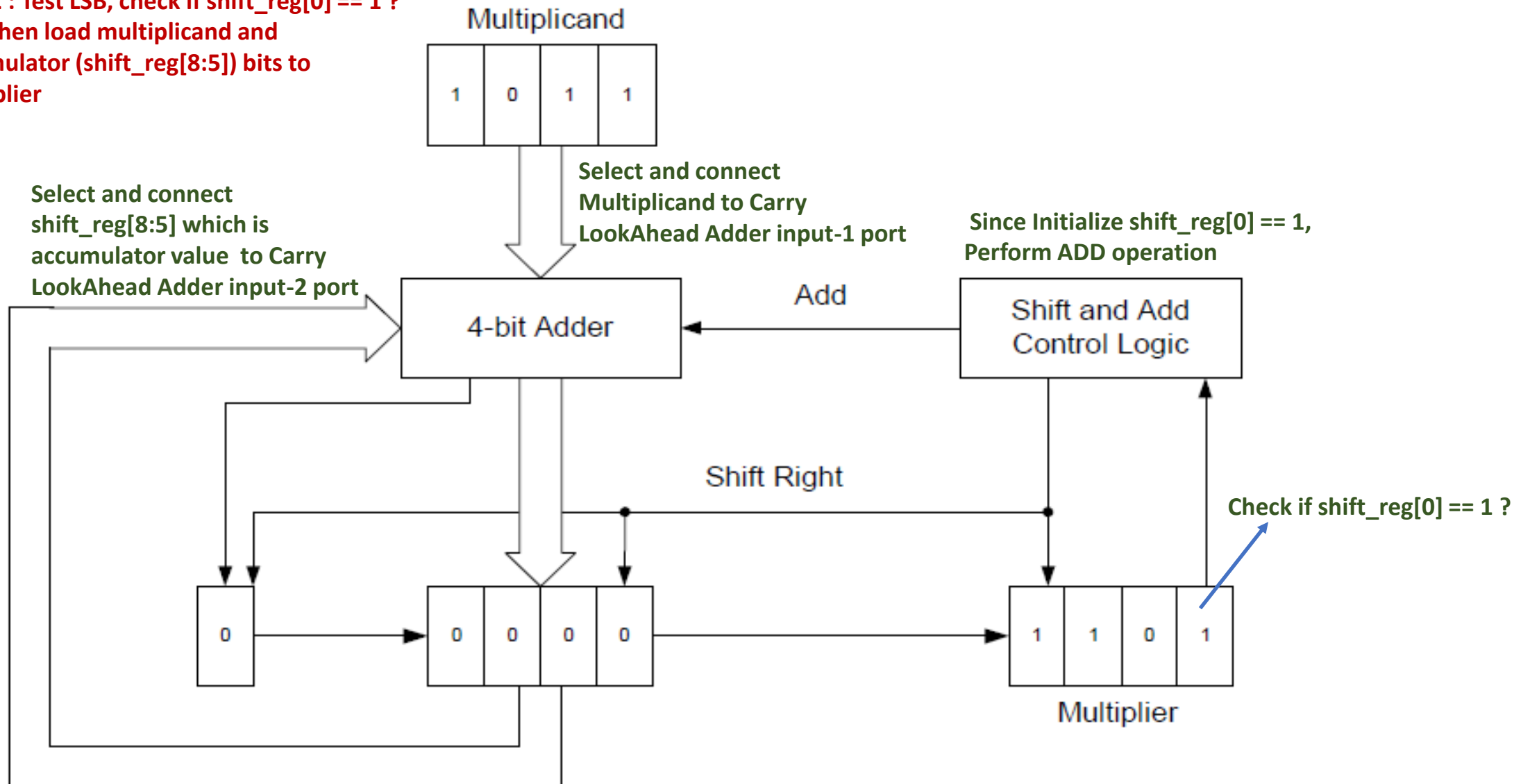
Step 2 : Test LSB, check if $\text{shift_reg}[0] == 1$?
If '1' then load multiplicand and accumulator (shift_reg[8:5]) bits to multiplier



N-bit counter value is still '0' at end of this step

SHIFT And ADD Integer Multiplier Algorithm Example Steps

Step 3 : Perform ADD Operation

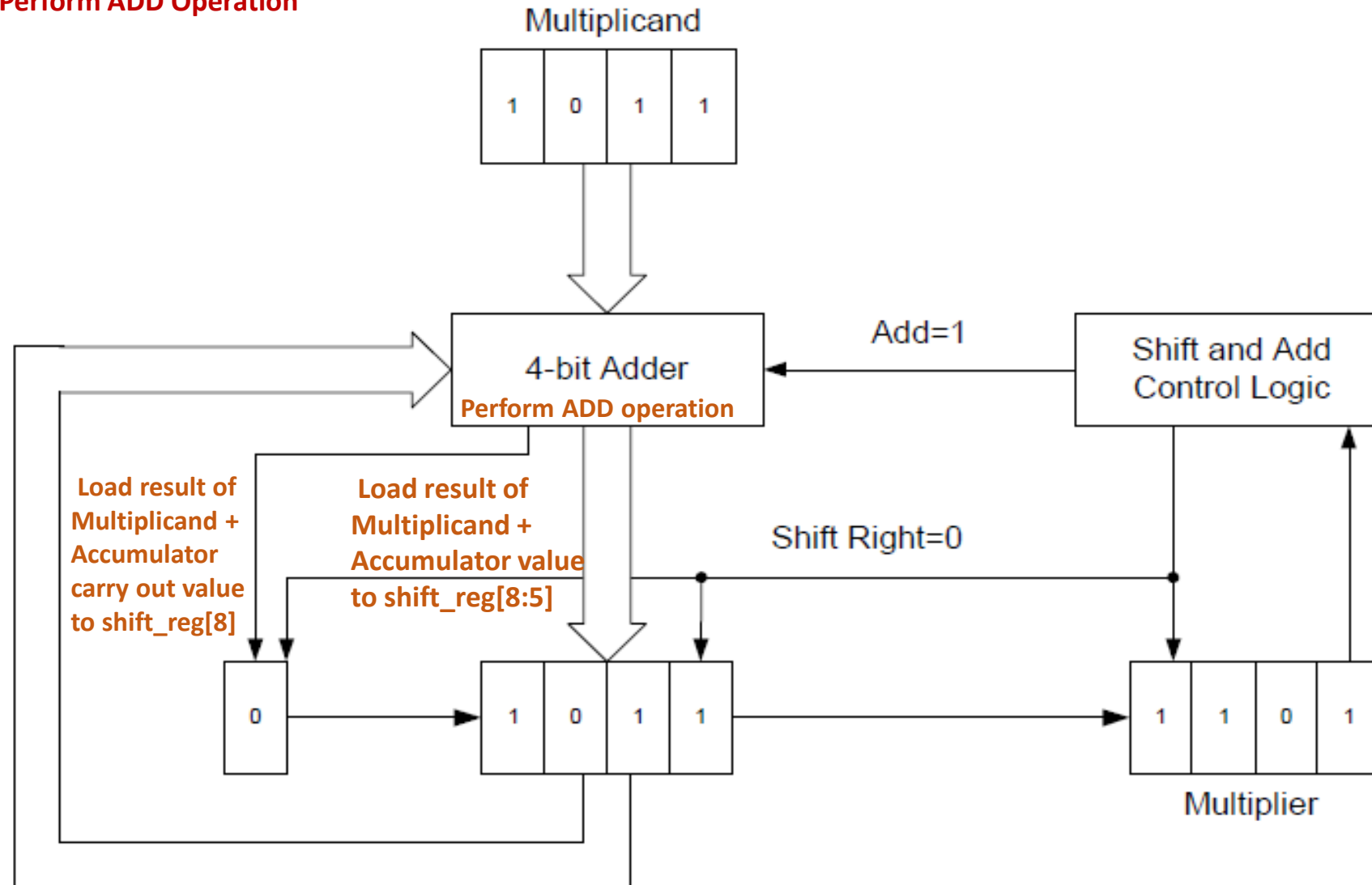


N-bit counter value is still '0' at end of this step

SHIFT And ADD Integer Multiplier Algorithm Example Steps

Step 4 : Perform SHIFT Operation

shifg_reg = shift_reg >> 1


And increment N-bit counter by 1

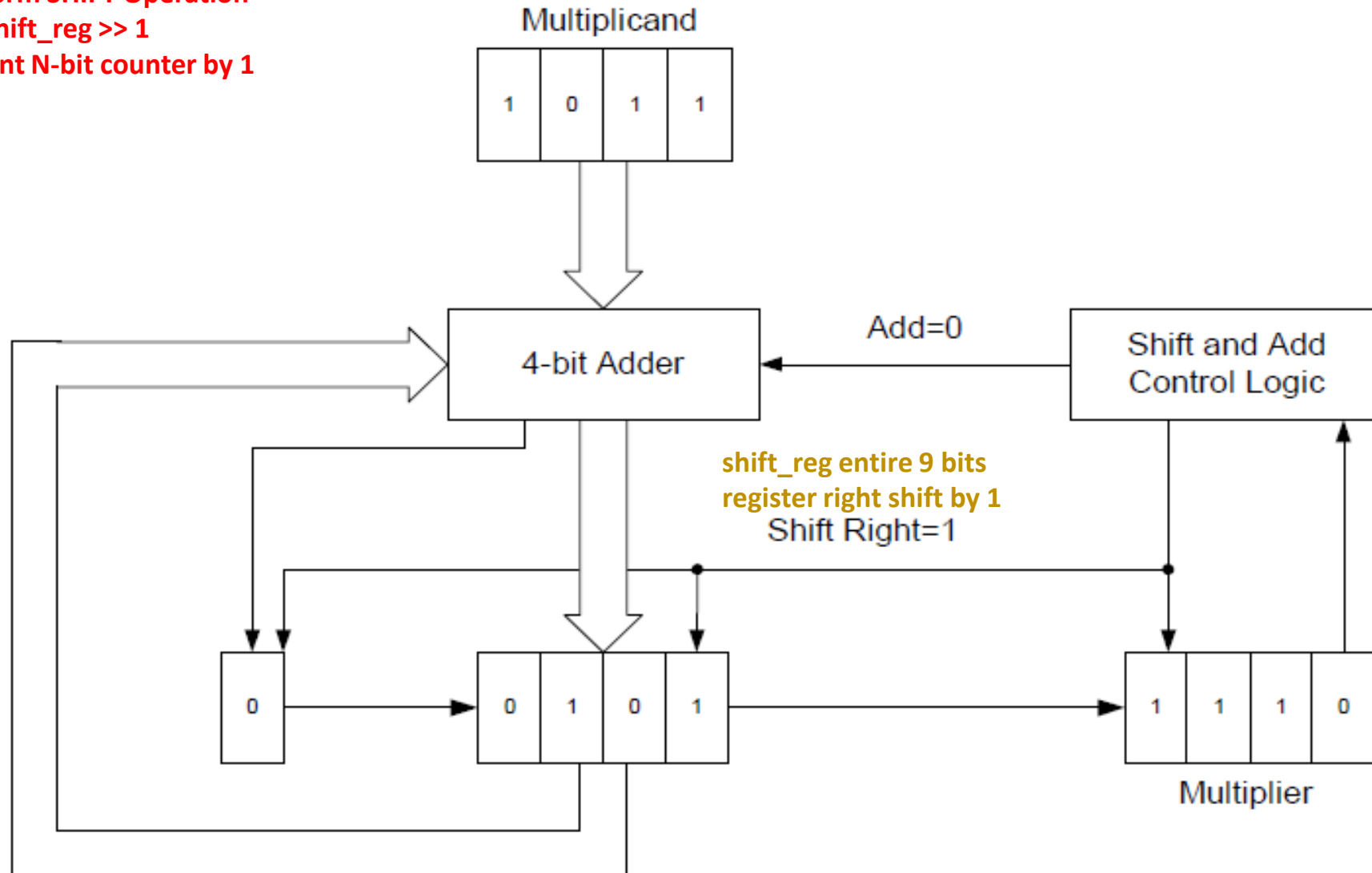

At end of N-bit count==0 stage, value of shift_reg = {0, 4'b0101, 4'b1110}

SHIFT And ADD Integer Multiplier Algorithm Example Steps

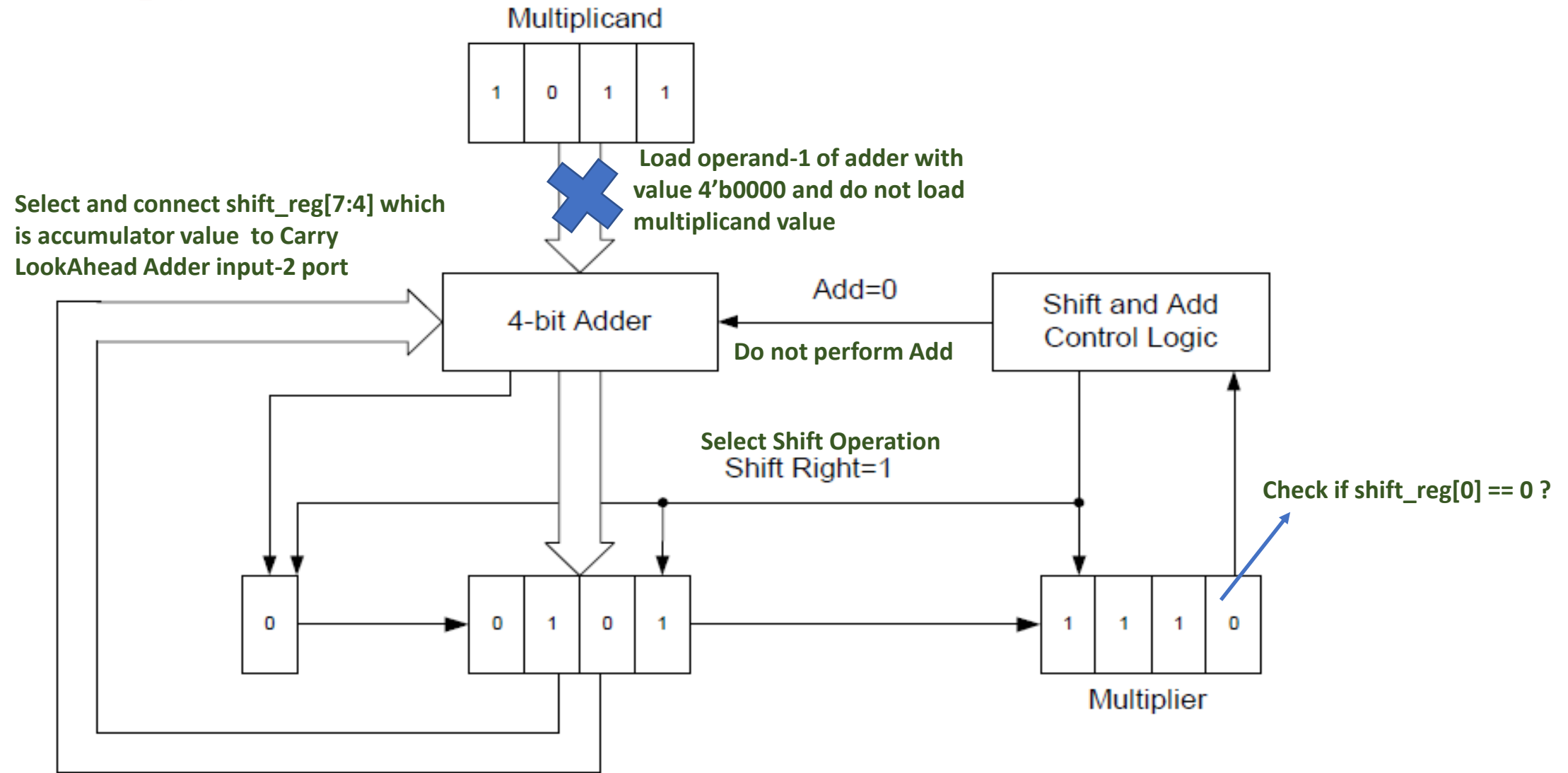Step 5 : Check if shift_reg[0] == 0 or 1 ?




N-bit Counter value is '1'

SHIFT And ADD Integer Multiplier Algorithm Example Steps

Step 6 : Perform SHIFT Operation

$\text{shifg_reg} = \text{shift_reg} \gg 1$

And increment N-bit counter by 1

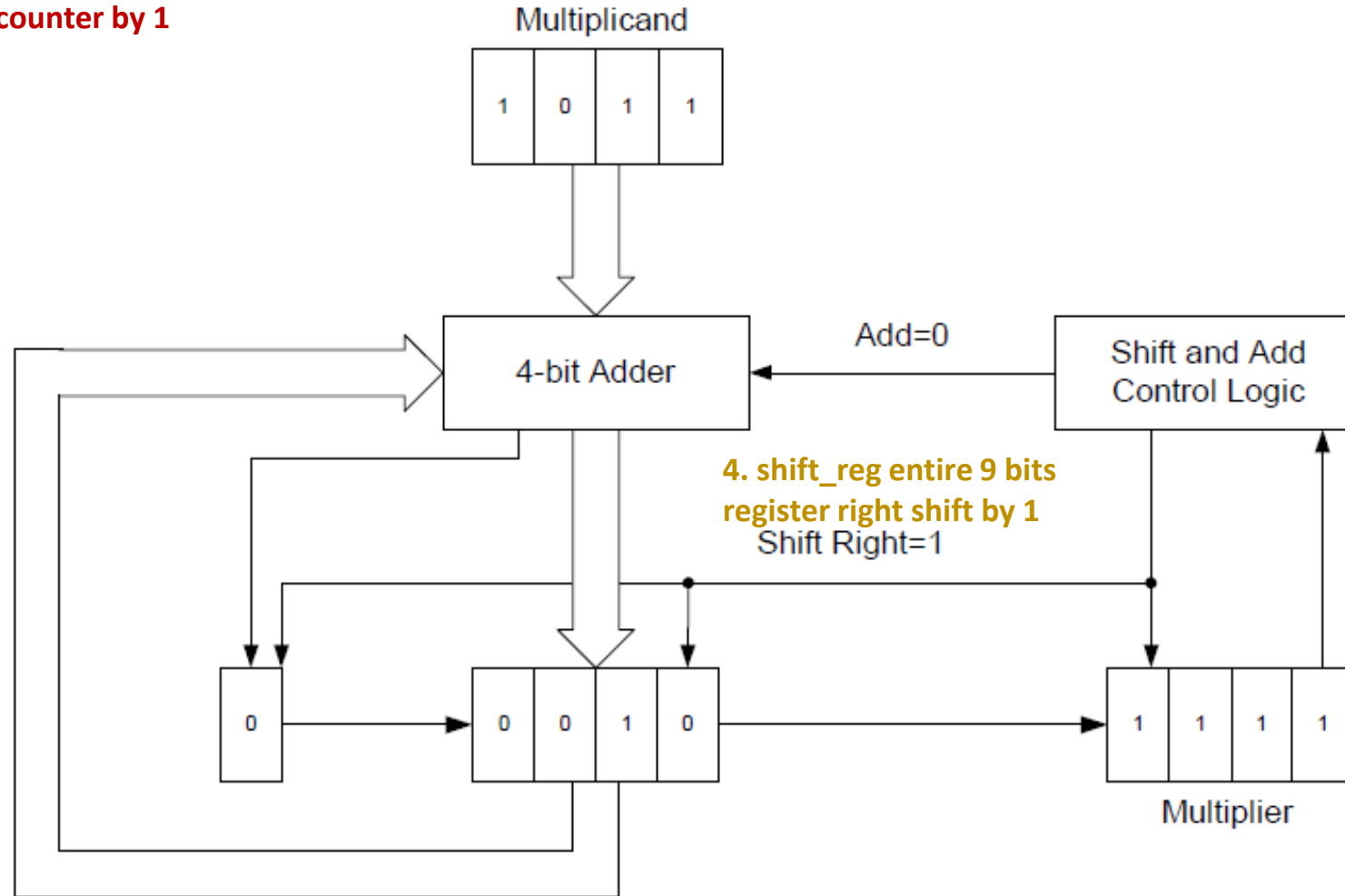


At end of N-bit count==1 stage, value of shift_reg = {0, 4'b0010, 4'b1111}

SHIFT And ADD Integer Multiplier Algorithm Example Steps

Step 7 : Check `shift_reg[0] == 1` or 0 ?

Step 8 : since `shift_reg[0] == 1`
then Perform Add Operation

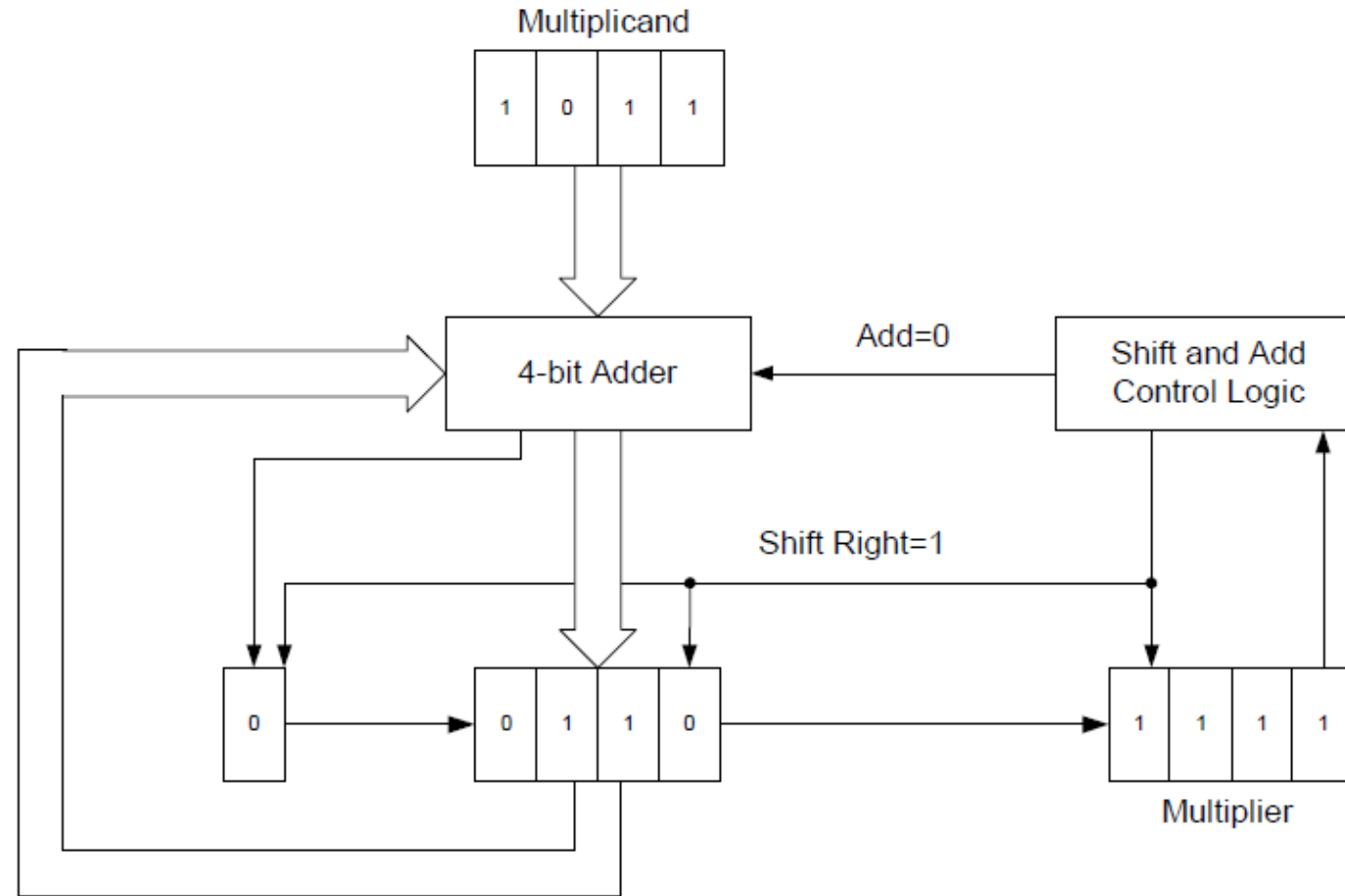Step 9 : Perform Shift operation
`shift_reg >> 1` and then increment
N-bit counter value




At end of N-bit count==2 stage, value of `shift_reg` = {0, 4'b0110, 4'b1111}

SHIFT And ADD Integer Multiplier Algorithm Example Steps

Step 10 : Check $\text{shift_reg}[0] == 1$ or 0 ?

Step 11 : since $\text{shift_reg}[0] == 1$
then Perform Add Operation

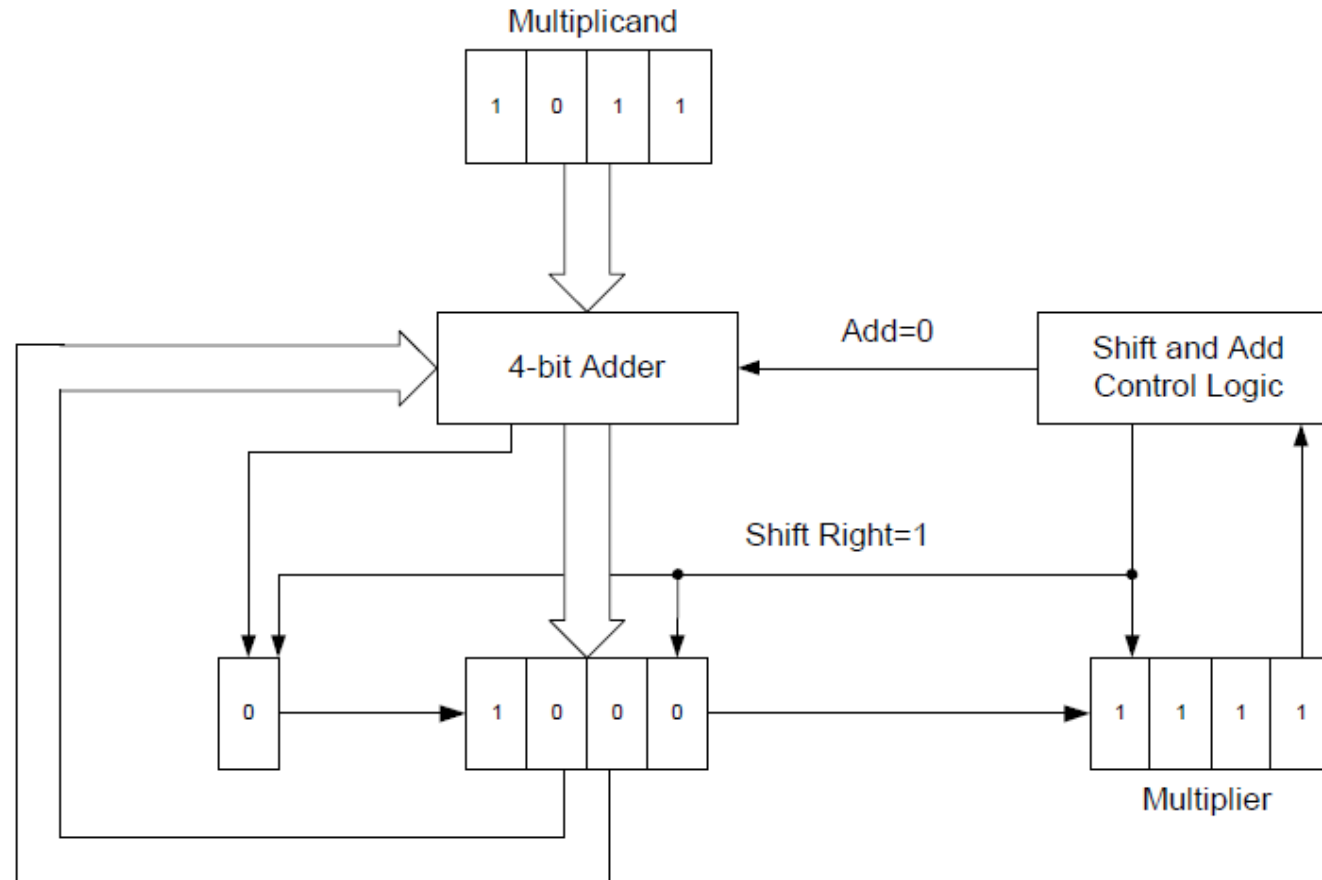Step 12 : Perform Shift operation
 $\text{shift_reg} \gg 1$ and then increment N-b
counter value



At end of N-bit count==3 stage, value of $\text{shift_reg} = \{0, 4'b1000, 4'b1111\}$
Since count == 3, set done = 1 and product = $\text{shift_reg} (9'b0_1000_1111) = 143$

Integer Multiplier Code Development Hint

❑ Define 6 FSM States

```
// next_state encoding and next_state variable
enum logic[2:0]{
    IDLE          = 3'b000,
    INITIALIZE    = 3'b001,
    TEST         = 3'b010,
    ADD          = 3'b011,
    SHIFT_AND_COUNT = 3'b100,
    DONE        = 3'b101
} next_state;
```

❑ For N-bit Integer Divider, ensure size of shift register is = $N + N + 1$ bits

- N bits to store adder output without carry out in shift register (**this is also known as accumulator**)
- N bits to store multiplier value
- 1 bit to store carryout bit from adder
- shift register format = {carryout, N-bit Adder output, N-bit Multiplier}

```
// Register to store Adder sum and multiplier
logic[(2*N):0] shift_reg;
```

❑ Use Carry Look Ahead Adder and Full Adder Module implementation from previous homework assignment

```
// Instantiate N-bit carry lookahead adder
// Pass add_operand1, add_operand2 and sum
// Tie CIN to '0'
carry_lookahead_adder #(N) adder_inst(

// Student to add code here
// use add_operand1, add_operand2, sum logic (wires) to connect to carry lookahead adder inputs

);
```

Integer Multiplier Code Development Hint

- ❑ Develop FSM code using single always block approach with non-blocking assignment statements within

```
always_ff@(posedge clock, posedge reset) begin
    if(reset) begin
        count <= 0;
        next_state <= IDLE;
        load_reg <= 0;
        shift_reg <= 0;
    end
    else begin
        case(next_state)
            // Intialized count, load_reg, shift reg to 0
            // Wait for start signal. if start is '1' then move to INITIALIZE otherwise stay in IDLE state
            IDLE: begin

                end
                // Load Multiplicand and Multiplier in a load register and a shift register
                // Initialize count to 0 and then set next_state to TEST
                INITIALIZE: begin

                end
                // Check shift register LSB and based on that perform ADD/Shift operation
                // if LSB='1' then perform ADD followed by Right Shift by 1
                // if LSB='0' then perform Right Shift by 1
                TEST: begin
                    if(shift_reg[0] == 1'b1) begin

                        end
                    else begin

                    end
                end
            end
        end
    end
end
```

Integer Multiplier Code Development Hint

❑ FSM code framework.... Continued

```
// Perform ADD operation
ADD: begin
    // Load shift register : Output sum from Adder which includes carry and retain previous lower bit of shift register
    // move to shift and increment count state (SHIFT_AND_COUNT)

end
// Perform Right Shift by 1 on shift_reg and check if count == N
SHIFT_AND_COUNT: begin
    // Right shift entire shift_reg by 1 position and store result in shift_reg
    // Increment count
    if(count == N-1) begin // If 'N' times SHIFT operation performed then move to Done state else go back to Test state

        end
    else begin

        end
    end
end
// Stay in DONE state for final product value to be available and done = 1
DONE: begin
    next_state <= IDLE; // Wait for right shift value to be available. This is the final product value.
end
endcase
end
```

❑ Using assign statement generate output 'done' and final 'product' value when FSM transitions to DONE state

```
// Generate done=1 when FSM reaches DONE state
assign done = (next_state == DONE) ? 1 : 0;

// Generate Product in DONE state by loading shift_reg value to it
assign product = (next_state == DONE) ? shift_reg : 0;
```