

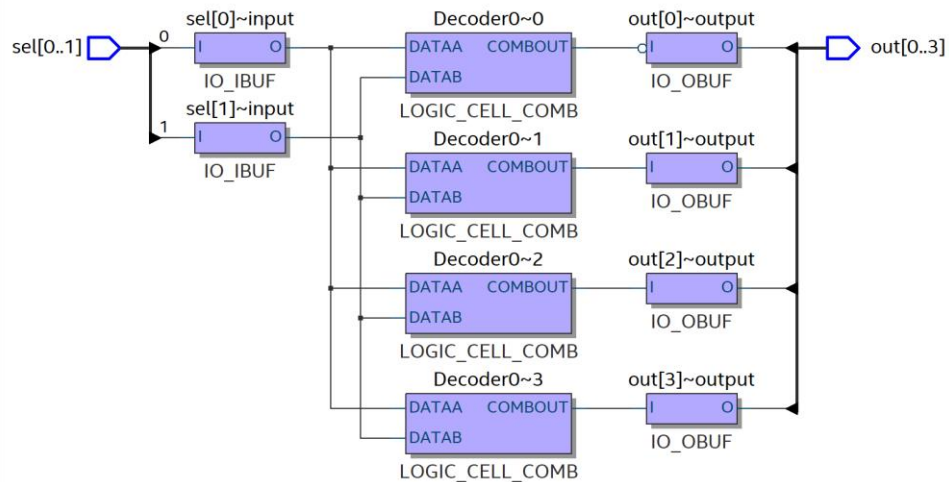


2-to-4 Decoder

Behavioral Level

```
1 // 2to4 decoder behavioral level code
2 module decoder(
3     input logic[1:0] sel,
4     output logic[3:0] out
5 );
6     always @(sel or out)
7     begin
8         case (sel)
9             2'b00 : out = 4'b0001;
10            2'b01 : out = 4'b0100;
11            2'b10 : out = 4'b0010;
12            2'b11 : out = 4'b1000;
13            default: out = 4'bzzzz;
14        endcase
15    end
16 endmodule
```

 

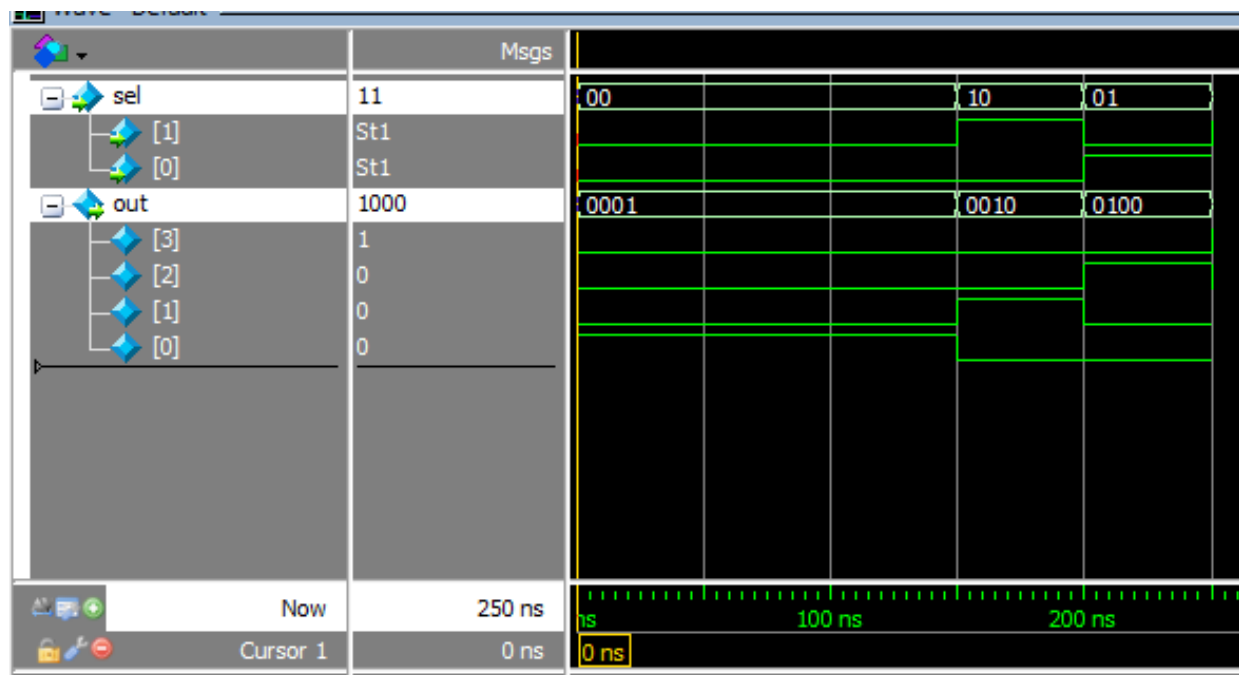

```
# Start time: 21:08:09 on Jan 13,2022
# Loading sv_std.std
# Loading work.decoder_2to4_testbench
# Loading work.decoder
add wave -r sim:/decoder_2to4_testbench/design_instance/*
VSIM 6> run -all
# time=0, sel=00 out=0001
#
# time=150, sel=10 out=0010
#
# time=200, sel=01 out=0100
#
# time=250, sel=11 out=1000
#
VSIM 7>
```



	Resource	Usage
1	▼ Estimated ALUTs Used	4
1	-- Combinational ALUTs	4
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	0
3		
4	▼ Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	4
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	4
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	4
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	4
12		
13	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	6
17		
18	DSP block 18-bit elements	0
19		

Dataflow Level

```



1 // 2to4 Decoder dataflow level code
2 module decoder(
3     input logic[1:0] sel,
4     output logic[3:0] out
5 );
6     assign out[0] = (!sel[0]) && (!sel[1]);
7     assign out[1] = (!sel[0]) && (sel[1]);
8     assign out[2] = (sel[0]) && (!sel[1]);
9     assign out[3] = (sel[0]) && (sel[1]);
10
11 endmodule

```

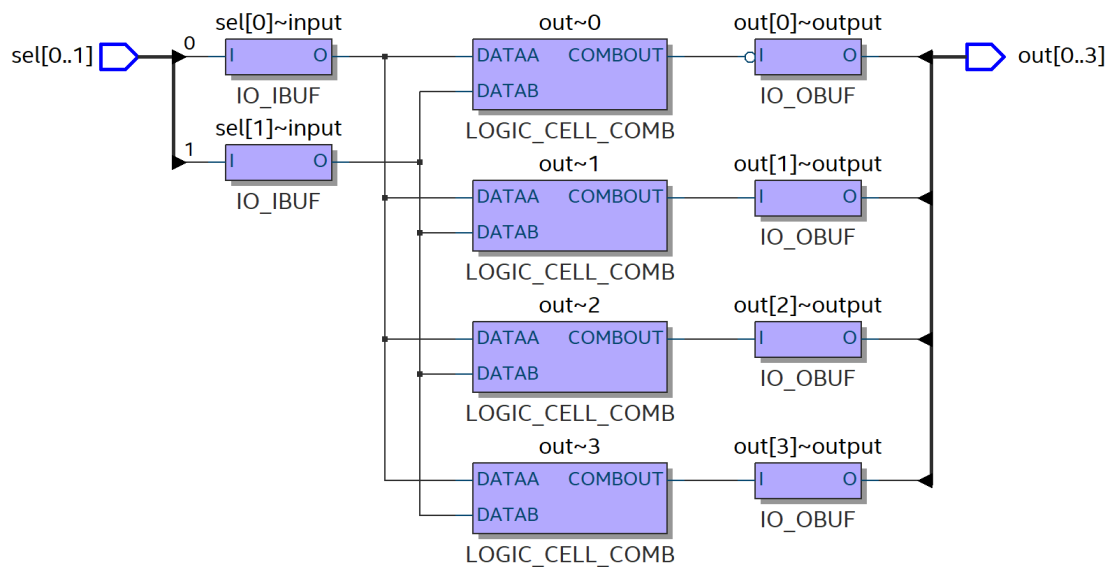 

	Resource	Usage
1	▼ Estimated ALUTs Used	4
1	-- Combinational ALUTs	4
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	0
3		
4	▼ Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	4
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	4
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	4
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	4
12		
13	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	6
17		
18	DSP block 18-bit elements	0
19		

Gate Level

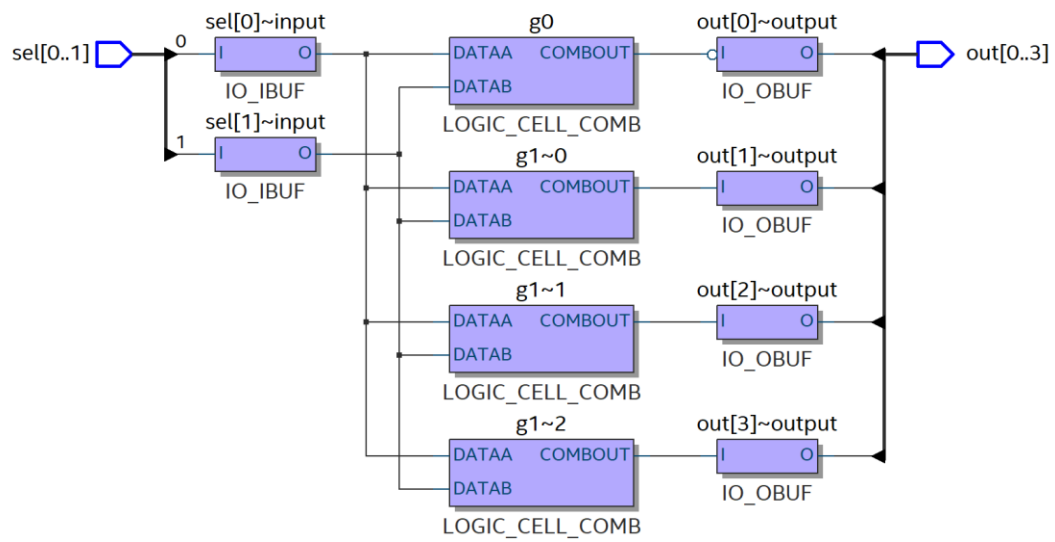 

	Resource	Usage
1	▼ Estimated ALUTs Used	4
1	-- Combinational ALUTs	4
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	0
3		
4	▼ Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	4
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	4
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	4
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	4
12		
13	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	6
17		
18	DSP block 18-bit elements	0
19		

Function of 2-to-4 decoder: Converts a 2-bit binary number into a 4-bit one-hot encoded representation, where the logical 1's index is representative of the input decimal number.

Number of ALUTs: 4 (6 I/O pins)



A 2-to-4 decoder can be implemented using 4 ALUTs because the 2-bit input has 4 unique states that is one hot encoded into a 4-bit output. Each bit of the output is tied to the output of one ALUT, thus four are needed in total.


Number of Functions: 4 (2 input, 1 output)

Each ALUT takes in the 2-bit input that can take on four unique states that represent 0-3 in decimal. The ALUT's memory is programmed in a way that will only output a logical 1 if the 2-bit input's state matches its predesignated output bit index. Since the same 2-bit input is fed into four ALUT's, and each ALUT outputs a bit, there are six I/O's.

MUX

Behavioral Level

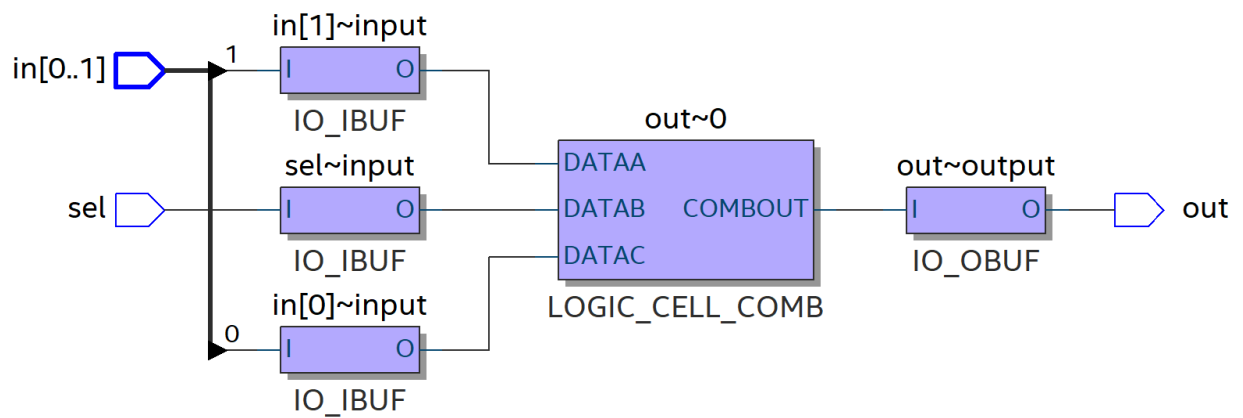
 


 

```
# Loading work.mux_2x1
add wave -r sim:/mux_2x1_testbench/design_instance/*
VSIM 6> run -all
# time=0, in=00 sel=0 out=0
#
# time=150, in=01 sel=0 out=1
#
# time=200, in=10 sel=0 out=0
#
# time=250, in=00 sel=1 out=0
#
# time=300, in=01 sel=1 out=0
#
# time=350, in=10 sel=1 out=1
#
VSIM 7>
```



1	▼ Estimated ALUTs Used	1
1	-- Combinational ALUTs	1
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	0
3		
4	▼ Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	1
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	1
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	1
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	1
12		
13	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	4
17		
18	DSP block 18-bit elements	0
19		

Dataflow Level

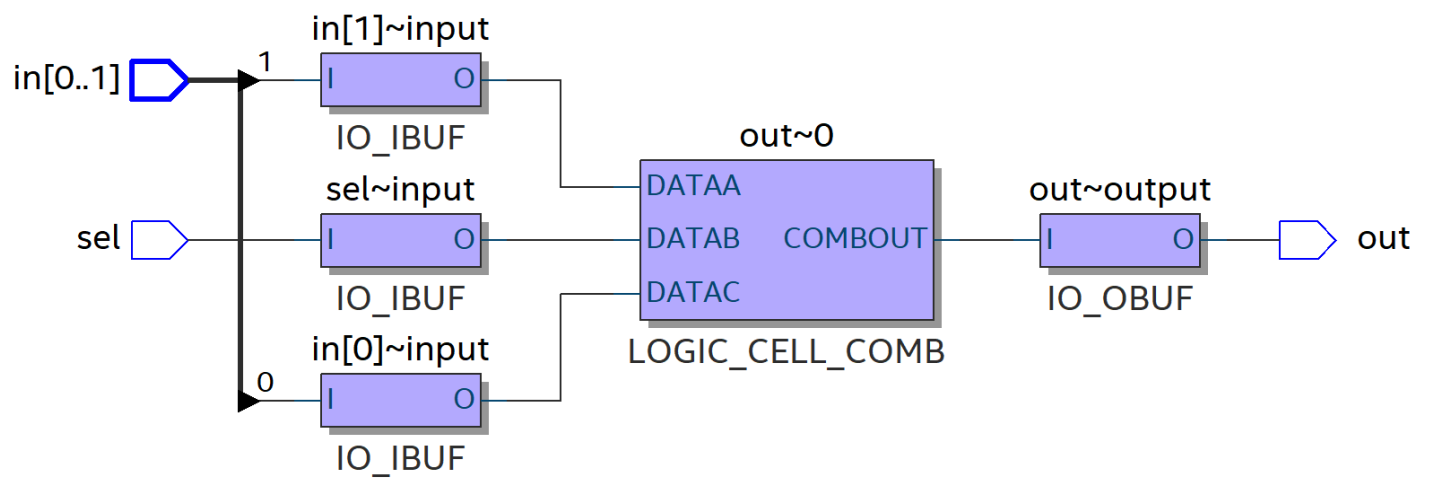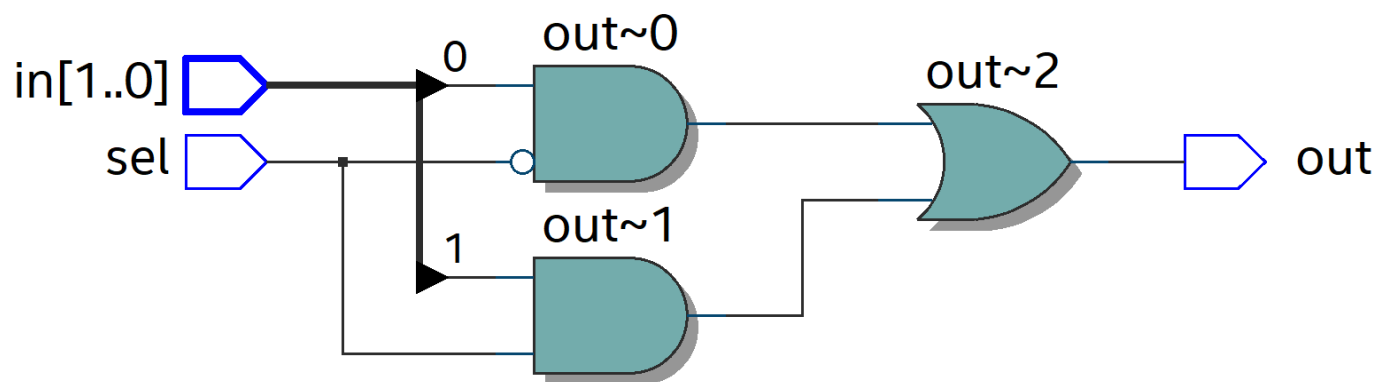

	Resource	Usage
1	▼ Estimated ALUTs Used	1
1	-- Combinational ALUTs	1
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	0
3		
4	▼ Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	1
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- ≤3 input functions	1
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	1
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	1
12		
13	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	4
17		
18	DSP block 18-bit elements	0
19		

Gate Level

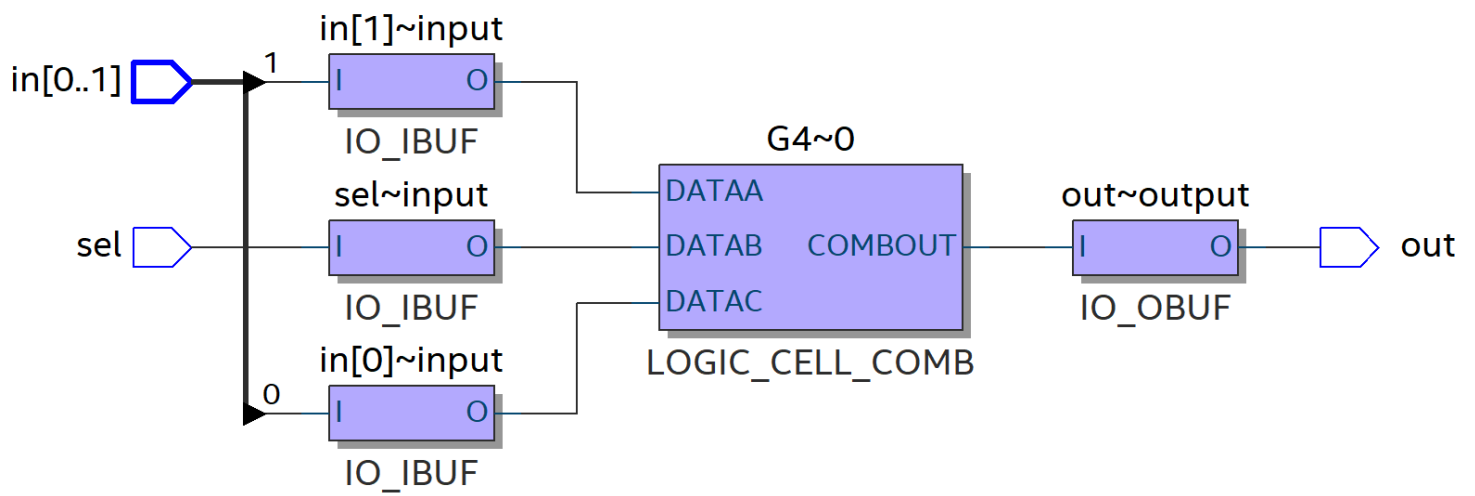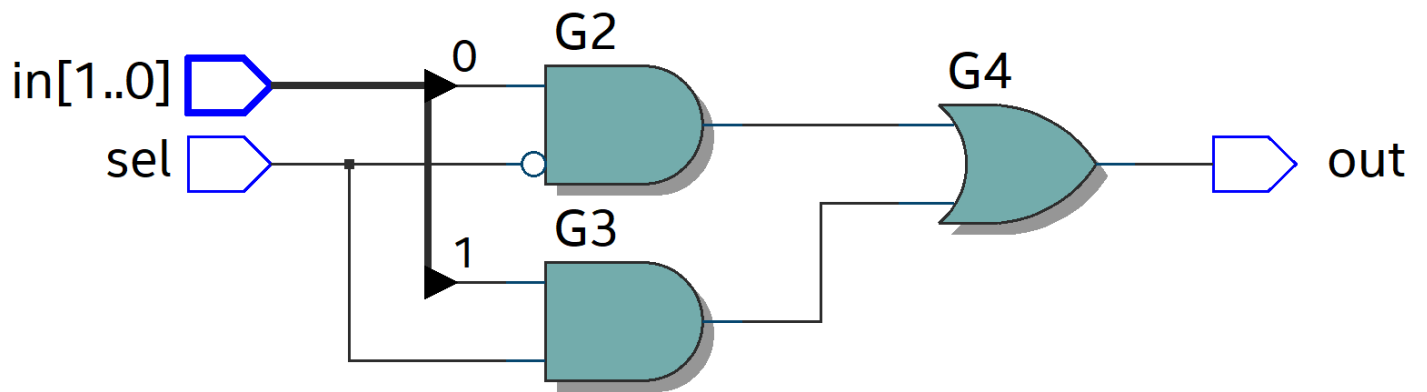

	Resource	Usage
1	▼ Estimated ALUTs Used	1
1	-- Combinational ALUTs	1
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	0
3		
4	▼ Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	1
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	1
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	1
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	1
12		
13	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	4
17		
18	DSP block 18-bit elements	0
19		

Function of 1-bit MUX: A two-line selector based on a 1-bit binary input. The 1-bit input's state changes which input line is to be selected and ported to the output i.e. 0 is first line and 1 is second line.

Number of ALUTs: 1 (4 I/O pins)



Since the MUX outputs only one bit, this can be accomplished with one ALUT with three inputs.


Number of Functions: 1 (3 input, 1 output)

2-bit input and 1-bit selector input equates to a 3-bit input Boolean expression. This can be one function that has one output. Overall, only one function is needed.

Full Adder

Behavioral Level

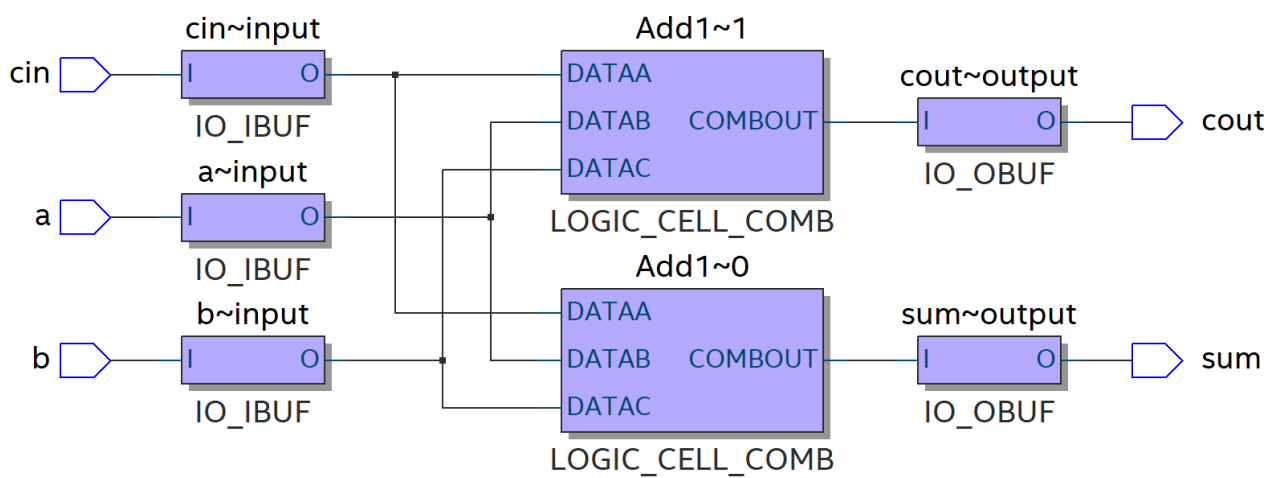
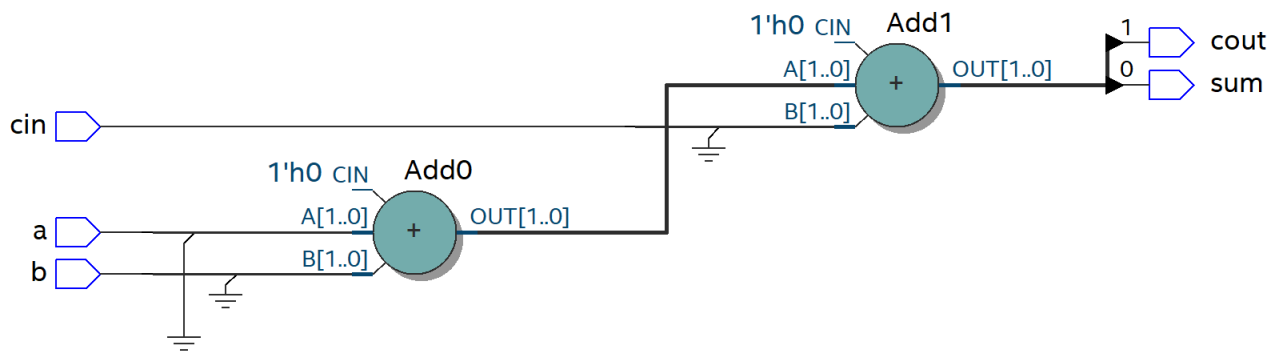


 

```
# Loading sv_std.std
# Loading work.fulladder_testbench
# Loading work.fulladder
add wave sim:/fulladder_testbench/design_instance/*
VSIM 6> run -all
# time=0    a=0    b=0    c=0    sum=0    cout=0
#
# time=150   a=1    b=0    c=0    sum=1    cout=0
#
# time=200   a=0    b=1    c=0    sum=1    cout=0
#
# time=250   a=1    b=1    c=0    sum=0    cout=1
#
# time=300   a=0    b=0    c=1    sum=1    cout=0
#
# time=350   a=1    b=0    c=1    sum=0    cout=1
#
# time=400   a=0    b=1    c=1    sum=0    cout=1
#
# time=450   a=1    b=1    c=1    sum=1    cout=1
#
VSIM 7>
```



	Resource	Usage
1	▼ Estimated ALUTs Used	2
1	-- Combinational ALUTs	2
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	0
3		
4	▼ Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	2
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	2
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	2
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	2
12		
13	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	5
17		
18	DSP block 18-bit elements	0
19		

Dataflow Level

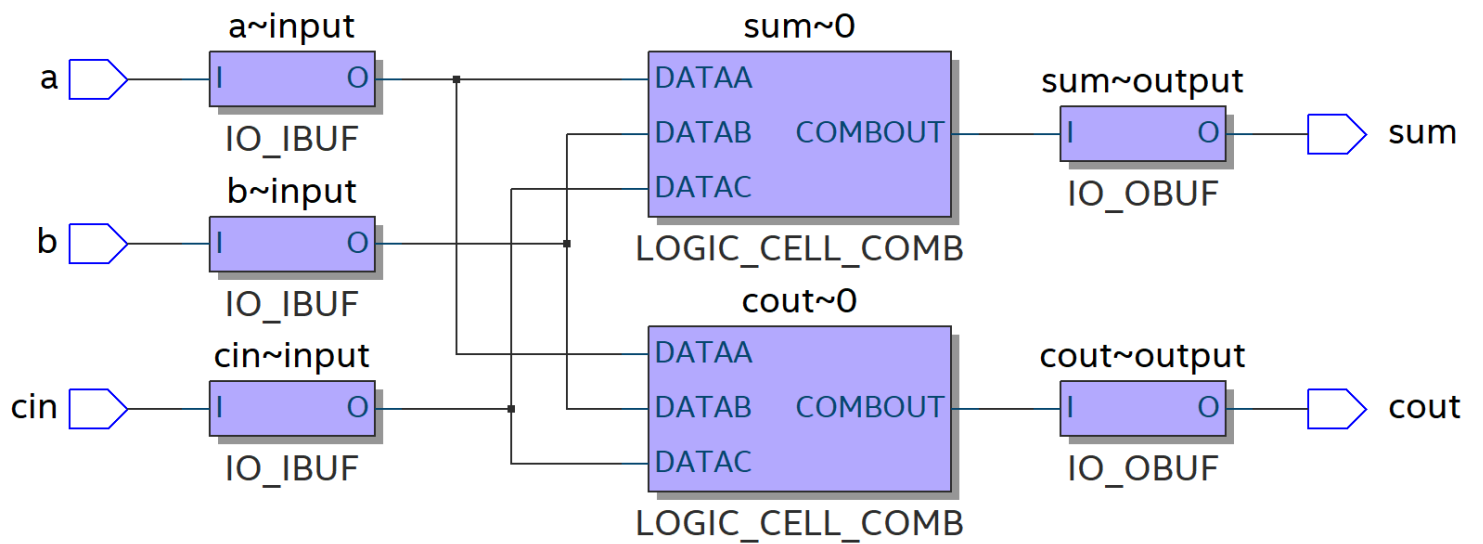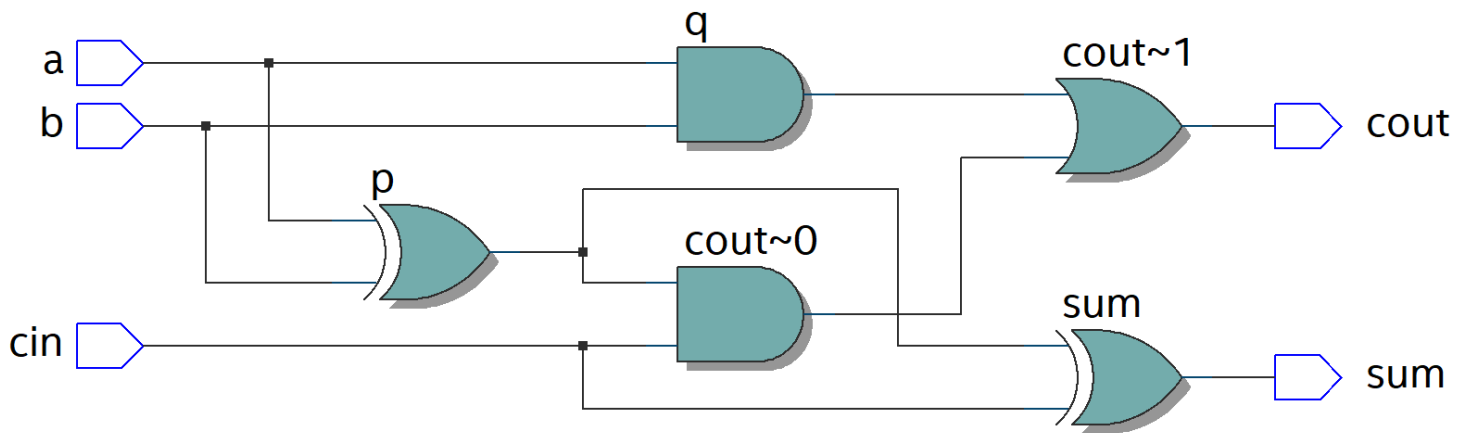

	Resource	Usage
1	▼ Estimated ALUTs Used	2
1	-- Combinational ALUTs	2
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	0
3		
4	▼ Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	2
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	2
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	2
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	2
12		
13	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	5
17		
18	DSP block 18-bit elements	0
19		

Gate Level

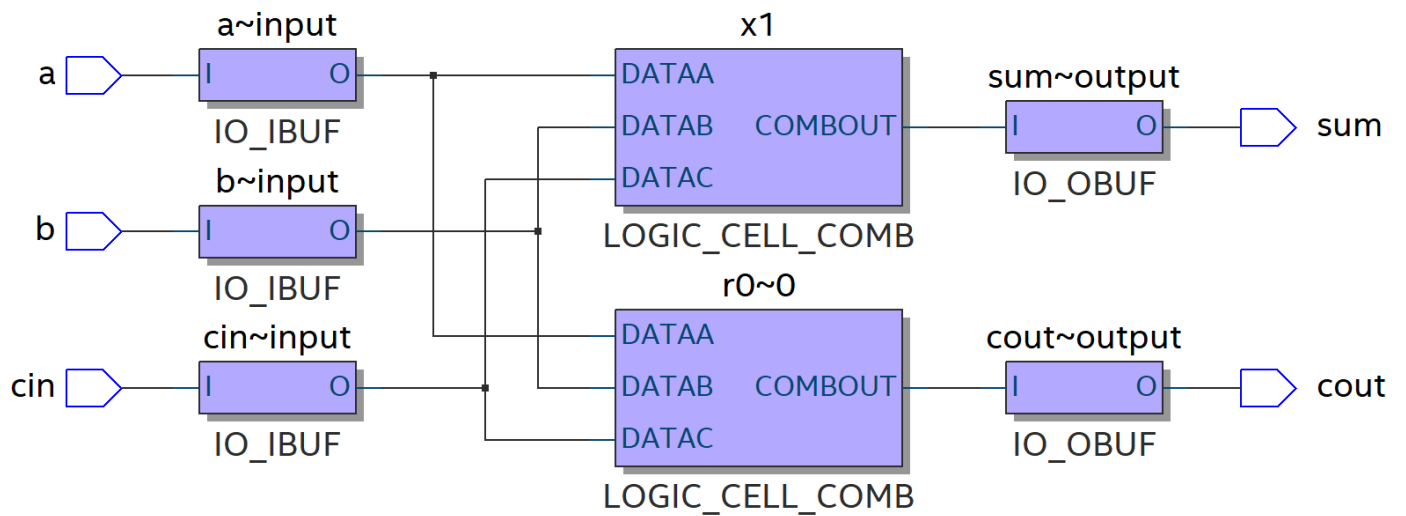 

	Resource	Usage
1	▼ Estimated ALUTs Used	2
1	-- Combinational ALUTs	2
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	0
3		
4	▼ Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	2
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	2
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	2
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	2
12		
13	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	5
17		
18	DSP block 18-bit elements	0
19		

Function of full adder: Adds two 1-bit operands and also takes in a 1-bit carry in. The result is two bits, one being the sum, and the other being the carry out. The sum and carry out represent the 2-bit result when the decimal result is larger than 1 that causes a bit overflow in sum.

Number of ALUTs: 2 (5 I/O pins)

Two distinct outputs are required: first between inputs a and b, second between a + b and carry in. This means a total of two ALUTs are needed.

Number of Functions: 2 (2 input, 1 output)

Two functions are needed – these are essentially half adders. Each half adder takes in two 1-bit inputs. The first half-adder's output is ported to the first input of the second half-adder. This is added to carry in. Overall, there are three inputs and 2 outputs, sum and carry out. A total of 5 I/O's are present.