

ECE 111 Winter 2022

HW6


Hao Le A15547504

## Moore Vending Machine

Code

```
1 // Vending Machine RTL Code
2 module vending_machine_moore(
3     input logic clk, rstn,
4     input logic N, D,
5     output logic open);
6
7 // state variables and state encoding parameters
8 parameter [1:0] CENTS_0=2'b00, CENTS_5=2'b01, CENTS_10=2'b10, CENTS_15=2'b11;
9 logic [1:0] present_state, next_state;
10
11 // Sequential Logic for present state
12 always_ff @(posedge clk) begin
13     if (!rstn) begin
14         present_state <= CENTS_0;
15     end
16     else begin
17         present_state <= next_state;
18     end
19 end
20
21 // Combination Logic for Next State and Output
22 always_comb begin
23     case(present_state)
24         CENTS_0:begin
25             open = 0;
26             if (D==1) begin
27                 next_state = CENTS_10;
28             end
29             else if (N==1) begin
30                 next_state = CENTS_5;
31             end
32             else begin
33                 next_state = CENTS_0;
34             end
35         end
36         CENTS_5:begin
37             open = 0;
38             if (D==1) begin
39                 next_state = CENTS_15;
40             end
41             else if (N==1) begin
42                 next_state = CENTS_10;
43             end
44             else begin
45                 next_state = CENTS_5;
46             end
47         end
48         CENTS_10:begin
49             open = 0;
50             if (D==1) begin
51                 next_state = CENTS_15;
52             end
53             else if (N==1) begin
54                 next_state = CENTS_15;
55             end
56             else begin
57                 next_state = CENTS_10;
58             end
59         end
60         CENTS_15:begin
61             open = 1;
62             if (rstn) begin
63                 next_state = CENTS_15;
64             end
65             else begin
66                 next_state = CENTS_0;
67             end
68         end
69         default:begin
70             next_state = CENTS_0;
71             open = 0;
72         end
73     endcase
74 end
75 endmodule: vending_machine_moore
```


RTL netlist

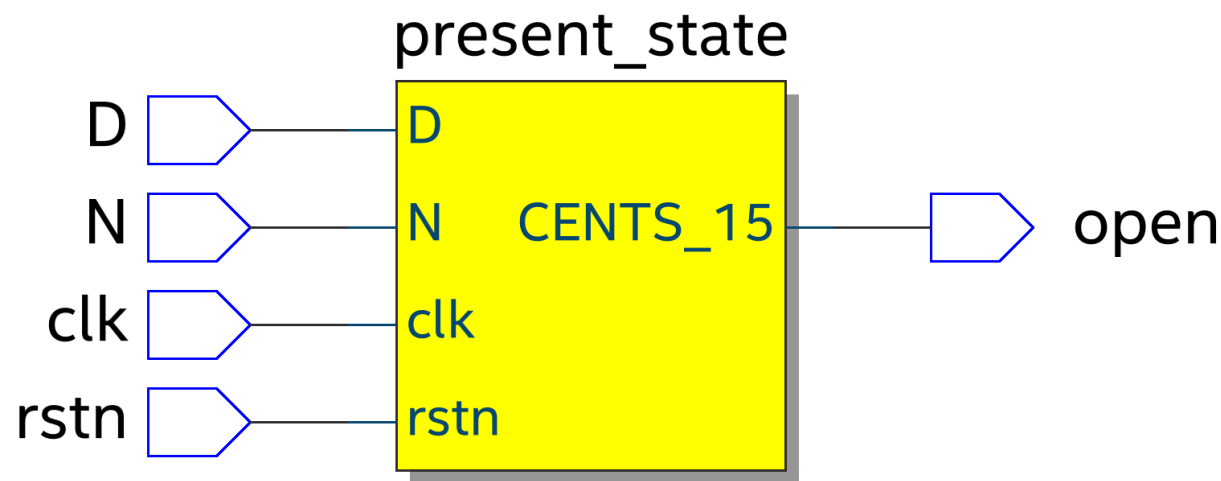

Resource usage


	resource	usage
1	Estimated ALUTs Used	4
1	-- Combinational ALUTs	4
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	4
3		
4	Estimated ALUTs Unavailable	2
1	-- Due to unpartnered combinational logic	2
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	4
7	Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	2
3	-- 5 input functions	1
4	-- 4 input functions	1
5	-- <=3 input functions	0
8		
9	Combinational ALUTs by mode	
1	-- normal mode	4
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	6
12		
13	Total registers	4
1	-- Dedicated logic registers	4
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	5
17		
18	DSP block 18-bit elements	0
19		

## State diagram

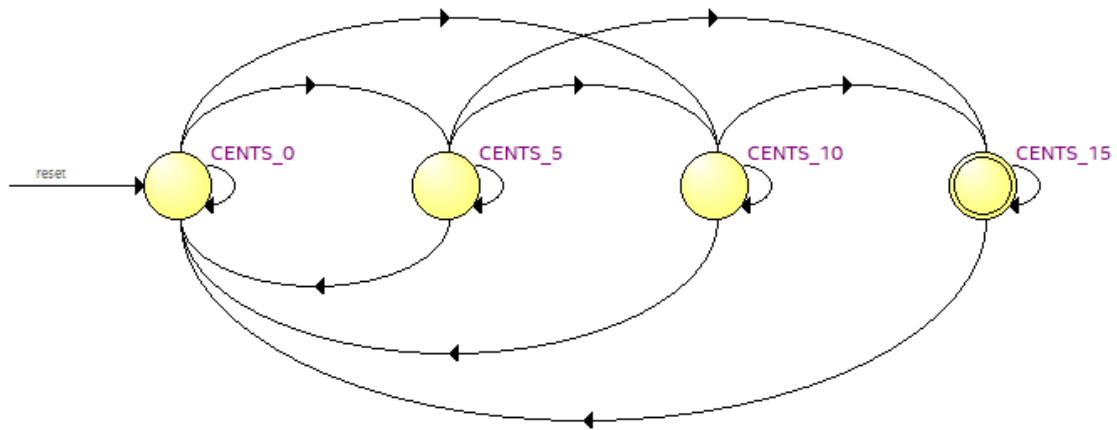

1	CENTS_0	CENTS_0	(!rstn) + (rstn).(!N).(!D)
2	CENTS_0	CENTS_10	(D).(rstn)
3	CENTS_0	CENTS_5	(N).(!D).(rstn)
4	CENTS_5	CENTS_0	(!rstn)
5	CENTS_5	CENTS_10	(N).(!D).(rstn)
6	CENTS_5	CENTS_15	(rstn).(D)
7	CENTS_5	CENTS_5	(!N).(!D).(rstn)
8	CENTS_10	CENTS_0	(!rstn)
9	CENTS_10	CENTS_10	(!N).(!D).(rstn)
10	CENTS_10	CENTS_15	(rstn).(!N).(D) + (rstn).(N)
11	CENTS_15	CENTS_0	(!rstn)
12	CENTS_15	CENTS_15	(rstn)

## Testbench simulation waveform

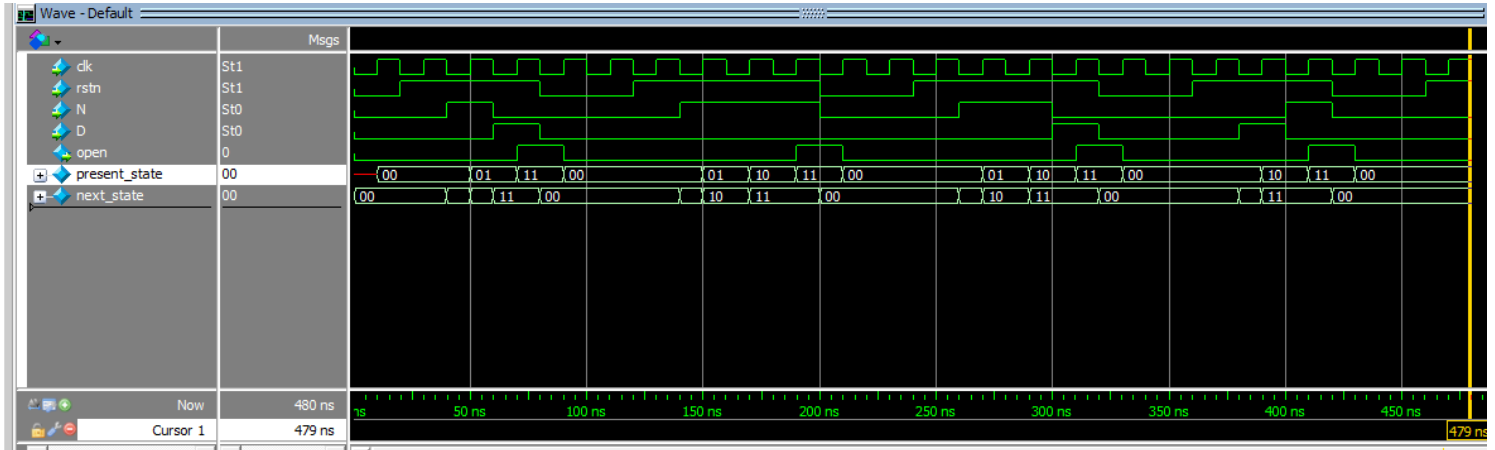


- A Moore state machine generates an output based on the current state, regardless of the inputs
- We see this behavior in the waveform; for example, in the first operation starting at around 30ns, a nickel is inserted, but since it was inserted at the falling edge of the clock, the state does not change from 00 to 01 (5 cents) until the next rising clock edge. We see this for the proceeding dime, where upon the rising edge, the state changes from 5 cents to 15 cents, thus bringing the output high
- This is distinct from a Mealy state machine in that the output did not go high immediately after the dime was inserted
- Lastly, once the 15 Cents (11) state has been reached, rstn goes low, but only at the rising clock edge does the present state switch back to 0 Cents, and the output goes low
- Described above is the correct behavior

# Mealy Vending Machine

## Code

```
1 // Vending Machine RTL Code
2 module vending_machine_mealy(
3     input logic clk, rstn,
4     input logic N, D,
5     output logic open);
6
7 // State encoding and state variables
8 parameter [1:0] CENTS_0=2'b00, CENTS_5=2'b01, CENTS_10=2'b10, CENTS_15=2'b11;
9 logic [1:0] present_state, next_state;
10
11 // Local variables for registering inputs N and D
12 logic r_N, r_D;
13
14 // Note : output open is not registered (i.e. no flipflop at output port open
15 // remember we learnt in class that mealy reacts immediately to change in inp
16 // Add flipflop for each input 'N' and 'D'
17 // Sequential Logic for present state
18 always_ff@(posedge clk) begin
19     if (!rstn) begin
20         present_state <= CENTS_0;
21         r_N <= 0;
22         r_D <= 0;
23     end
24     else begin
25         r_N <= N;
26         r_D <= D;
27         present_state <= next_state;
28     end
29 end
30
31 // Combination Logic for Next State and Output
32 always_comb begin
33     case(present_state)
34
35         CENTS_0:begin
36             if (r_D==1) begin
37                 next_state = CENTS_10;
38                 open = 0;
39             end
40             else if (r_N==1) begin
41                 next_state = CENTS_5;
42                 open = 0;
43             end
44             else begin
45                 next_state = CENTS_0;
46                 open = 0;
47             end
48         end
49
50         CENTS_5:begin
51             if (r_D==1) begin
52                 next_state = CENTS_15;
53                 open = 1;
54             end
55             else if (r_N==1) begin
56                 next_state = CENTS_10;
57                 open = 0;
58             end
59             else begin
60                 next_state = CENTS_5;
61                 open = 0;
62             end
63         end
64
65         CENTS_10:begin
66             if (r_D==1) begin
67                 next_state = CENTS_15;
68                 open = 1;
69             end
70             else if (r_N==1) begin
71                 next_state = CENTS_15;
72                 open = 1;
73             end
74             else begin
75                 next_state = CENTS_10;
76                 open = 0;
77             end
78         end
79
80         CENTS_15:begin
81             if (rstn) begin
82                 next_state = CENTS_15;
83                 open = 1;
84             end
85             else begin
86                 next_state = CENTS_0;
87                 open = 0;
88             end
89         end
90
91         default:begin
92             next_state = CENTS_0;
93             open = 0;
94         end
95     endcase
96 end
97 endmodule: vending_machine_mealy
```


RTL netlist

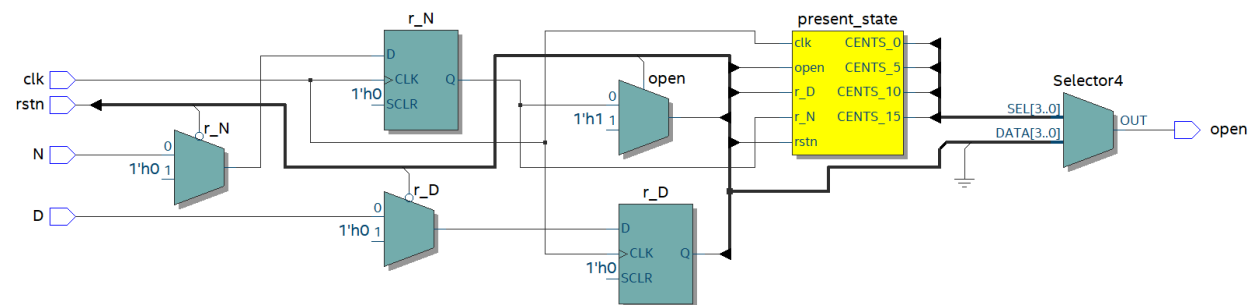

Resource usage


	Resource	Usage
1	Estimated ALUTs Used	7
1	-- Combinational ALUTs	7
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	6
3		
4	Estimated ALUTs Unavailable	3
1	-- Due to unpartnered combinational logic	3
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	7
7	Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	3
3	-- 5 input functions	1
4	-- 4 input functions	1
5	-- <=3 input functions	2
8		
9	Combinational ALUTs by mode	
1	-- normal mode	7
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	10
12		
13	Total registers	6
1	-- Dedicated logic registers	6
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	5
17		
18	DSP block 18-bit elements	0

## State diagram

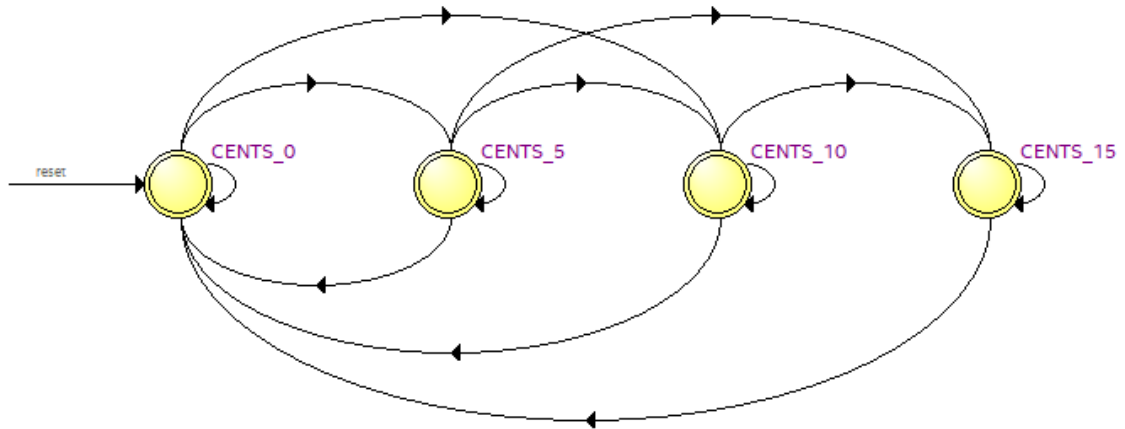

	Source State	Destination State	Condition
1	CENTS_0	CENTS_10	(r_D).(rstn)
2	CENTS_0	CENTS_5	(r_N).(!r_D).(rstn)
3	CENTS_0	CENTS_0	(!rstn) + (rstn).(!r_N).(!r_D)
4	CENTS_5	CENTS_15	(rstn).(r_D)
5	CENTS_5	CENTS_10	(r_N).(!r_D).(rstn)
6	CENTS_5	CENTS_5	(!r_N).(!r_D).(rstn)
7	CENTS_5	CENTS_0	(!rstn)
8	CENTS_10	CENTS_15	(rstn).(open)
9	CENTS_10	CENTS_10	(!r_N).(!r_D).(rstn)
10	CENTS_10	CENTS_0	(!rstn)
11	CENTS_15	CENTS_15	(rstn)
12	CENTS_15	CENTS_0	(!rstn)

Testbench simulation waveform

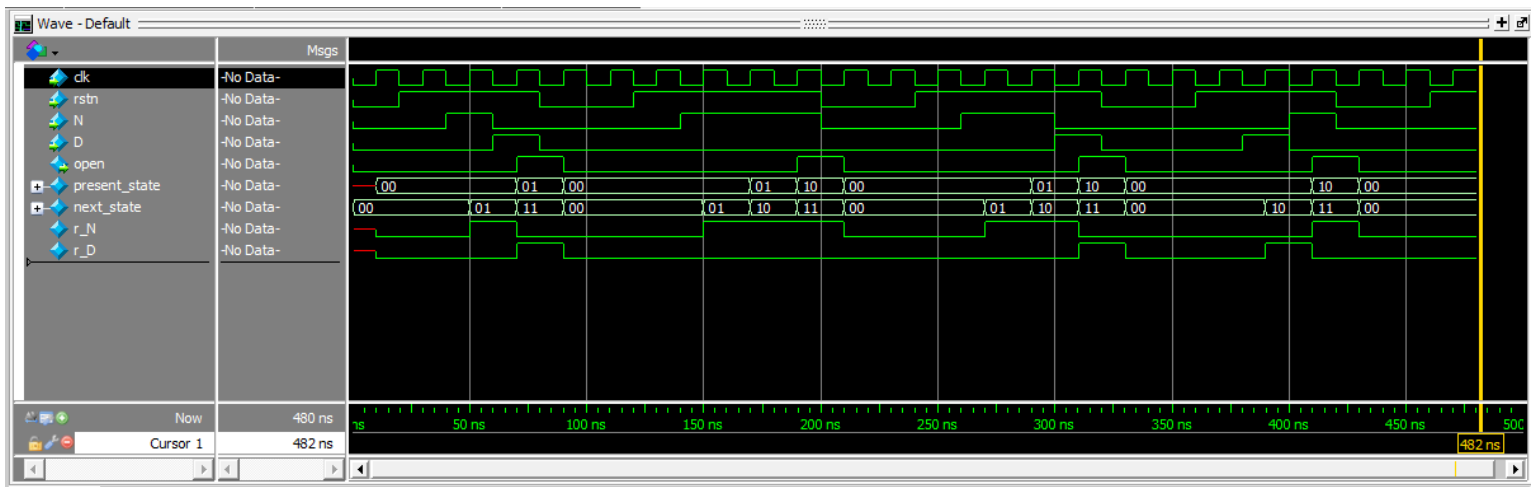

- A Mealy state machine generates an output based on the present state and the inputs; this differs from a Moore in that the output reacts immediately to a changing input
- In this implementation, flip flops were added to the inputs to delay them by half a clock cycle; this is to remedy the issue of double counting, especially during the third operation of the vending machine at around 260ns. As a side effect, the actual operation of this state machine is exactly like a Moore
- Without the flip flops, the inserted nickel would be counted three times, thus triggering the output before the dime even gets inserted which is incorrect behavior
- The “ideal” inputs would be the outputs of the registers
- Focusing on r\_N and r\_D as the inputs now, we see that at 50ns, the first nickel gets inserted, and the state is changed to 01 (5 Cents) at the positive clock edge
- Then, a dime is inserted, and the state changes to 11 (15 Cents) at the next positive clock edge
- We also observe that the output goes high as soon as the dime is inserted even though at that point, the present state is still 01 (5 Cents)
- This is because the Mealy machine knows the next state will be 15 Cents, so it triggers the output beforehand, saving a clock cycle.
- Described above is the correct behavior, assuming the inputs are timed correctly




# Integer Multiplier

## Code

```
1 timescale 1ns/1ps
2 // include "carry_lookahead_adder.sv"
3
4 module integer_multiplier // Module start declaration
5 # (parameter N=4) // Parameter declaration
6
7 input clock, reset, start,
8 input logic[N-1:0] multiplicand, multiplier,
9 output logic[(2*N):0] product,
10 output logic done
11
12
13 // Count variable for ADD/SHIFT stages
14 logic [$clog2(N)-1:0] count;
15
16 // Register to load multiplicand value
17 logic[N-1:0] load_reg;
18
19 // Register to store Adder sum and multiplier
20 logic[(2*N):0] shift_reg;
21
22 // wires to connect with carry lookahead adder
23 logic[N-1:0] add_operand1, add_operand2;
24 logic[N:0] sum;
25
26 // next_state encoding and next_state variable
27 enum logic[2:0] {
28     IDLE = 3'b000,
29     INITIALIZE = 3'b001,
30     TEST = 3'b010,
31     ADD = 3'b011,
32     SHIFT_AND_COUNT = 3'b100,
33     DONE = 3'b101
34 } next_state;
35
36 // Instantiate N-bit carry lookahead adder
37 // Pass add_operand1, add_operand2 and sum
38 // Tie CIN to '0'
39
40 carry_lookahead_adder #(N(N)) adder_inst (
41     .A(add_operand1),
42     .B(add_operand2),
43     .CIN(1'b0),
44     .result(sum)
45 );
46
47 // Control FSM for Integer Multiplier
48 // use single always block FSM approach
49 // use "only" non-blocking assignment statements within always block
50 always_ff @(posedge clock, posedge reset) begin
51     if (reset) begin
52         count <= 0;
53         next_state <= IDLE;
54         load_reg <= 0;
55         shift_reg <= 0;
56     end
57     else begin
58         case (next_state)
59         IDLE: begin
60             if (!start) begin
61                 next_state <= IDLE;
62             end
63             else begin
64                 next_state <= INITIALIZE;
65             end
66         INITIALIZE: begin
67             count <= 0;
68             shift_reg <= {1'b0, {N{1'b0}}, multiplier};
69             next_state <= TEST;
70         TEST: begin
71             if (shift_reg[0] == 1'b1) begin
72                 add_operand1 <= multiplicand;
73                 add_operand2 <= shift_reg[(2*N)-1:N];
74                 next_state <= ADD;
75             end
76             else begin
77                 add_operand1 <= 0;
78                 add_operand2 <= shift_reg[(2*N)-1:N];
79                 next_state <= SHIFT_AND_COUNT;
80             end
81         ADD: begin
82             shift_reg <= {sum, shift_reg[N-1:0]};
83             next_state <= SHIFT_AND_COUNT;
84         SHIFT_AND_COUNT: begin
85             if (count == N-1) begin
86                 shift_reg <= shift_reg >> 1;
87                 next_state <= DONE;
88             end
89             else begin
90                 shift_reg <= shift_reg >> 1;
91                 count <= count + 1;
92                 next_state <= TEST;
93             end
94         DONE: begin
95             next_state <= IDLE;
96         end
97     end
98 end
99
100
101
102
103
104
105
106
107
108
109
110
111
112
113
114
115
116
117
118
119
120
121
122
123
124
125
126
127
128
129
130
131
132 // Generate done=1 when FSM reaches DONE state
133 assign done = (next_state == DONE) ? 1 : 0;
134
135 // Generate Product in DONE state by loading shift_reg value to it
136 assign product = (next_state == DONE) ? shift_reg : 0;
137
138 endmodule: integer_multiplier
139
140
141
999
```


RTL netlist

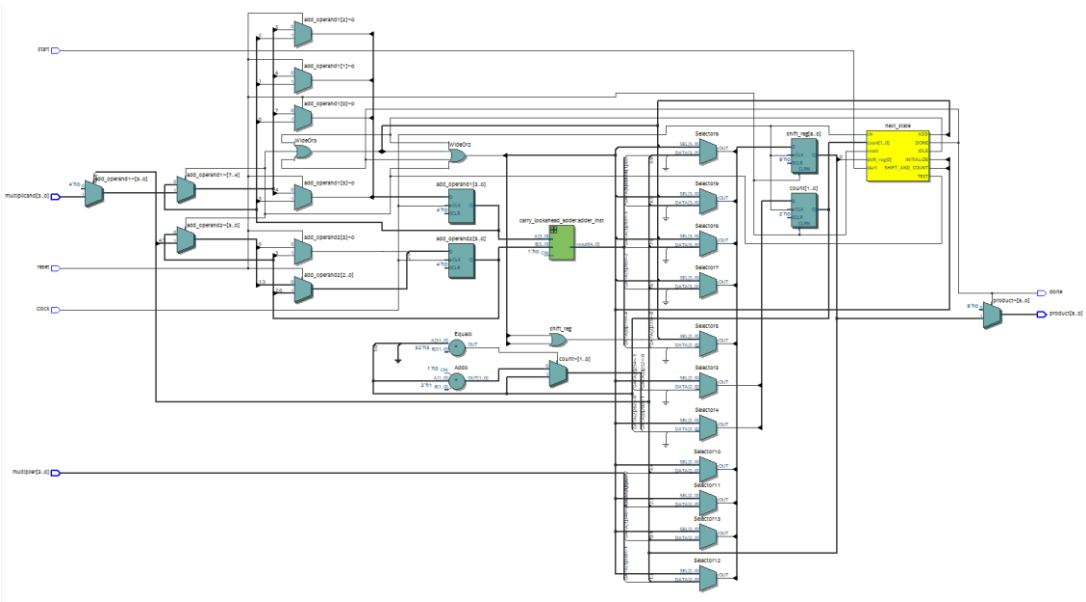

Resource usage



	Resource	Usage
1	Estimated ALUTs Used	38
1	-- Combinational ALUTs	38
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	25
3		
4	Estimated ALUTs Unavailable	1
1	-- Due to unpartnered combinational logic	1
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	38
7	Combinational ALUT usage by number of inputs	
1	-- 7 input functions	1
2	-- 6 input functions	2
3	-- 5 input functions	2
4	-- 4 input functions	7
5	-- <=3 input functions	26
8		
9	Combinational ALUTs by mode	
1	-- normal mode	37
2	-- extended LUT mode	1
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	42
12		
13	Total registers	25
1	-- Dedicated logic registers	25
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	21
17		
18	DSP block 18-bit elements	0
19		

## State diagram

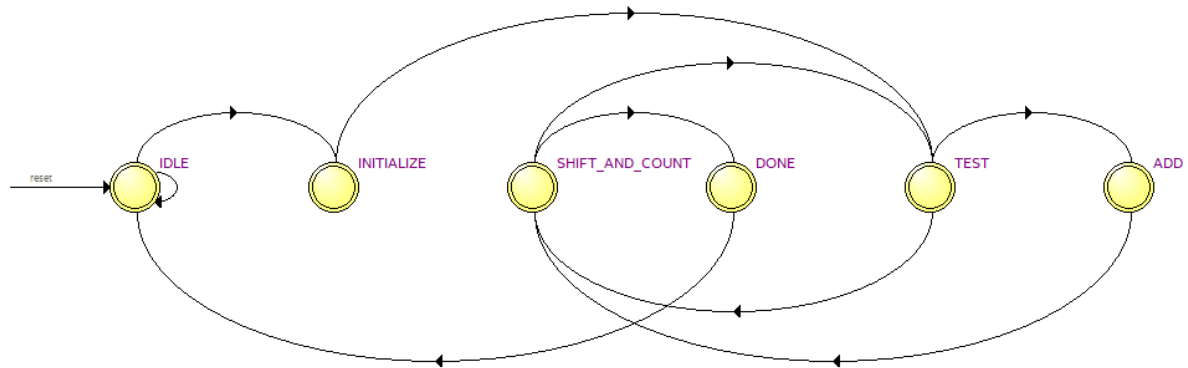

	Source State	Destination State	Condition
1	ADD	SHIFT_AND_COUNT	
2	DONE	IDLE	
3	IDLE	INITIALIZE	(start)
4	IDLE	IDLE	(!start)
5	INITIALIZE	TEST	
6	SHIFT_AND_COUNT	TEST	(!count[0]) + (count[0]).(!count[1])
7	SHIFT_AND_COUNT	DONE	(count[0]).(count[1])
8	TEST	SHIFT_AND_COUNT	(!shift_reg[0])
9	TEST	ADD	(shift_reg[0])

## Testbench simulation waveform

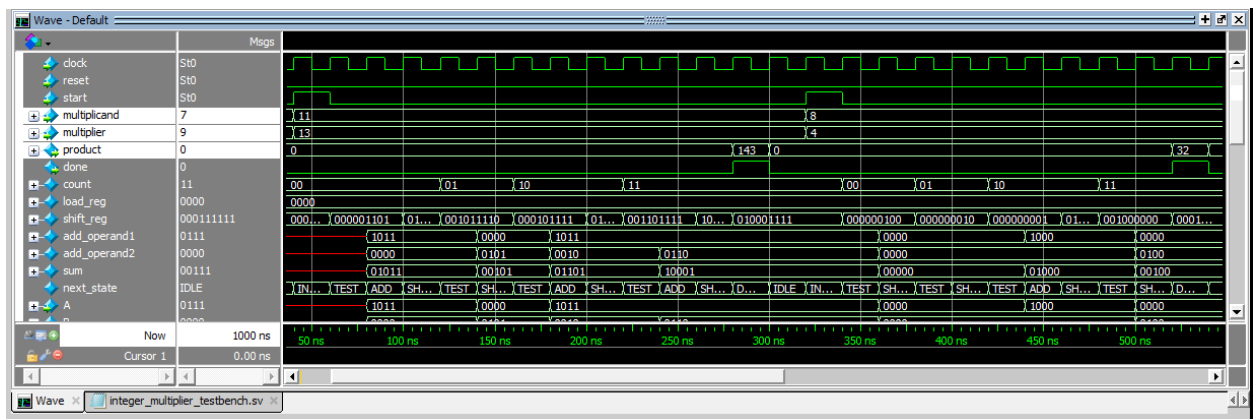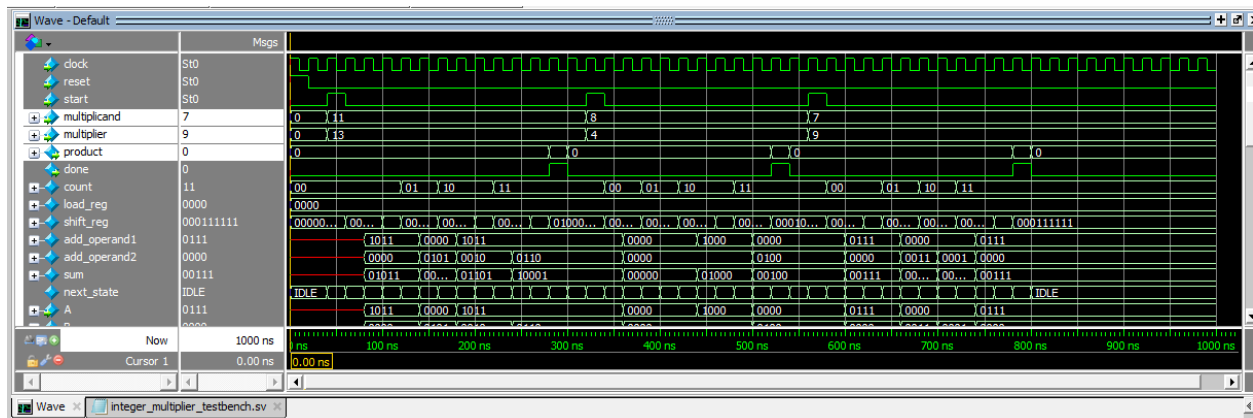

```

VSIM8> run -all
# time=280000 Multiplicand=11 Multiplier=13 Product=143 Done=1 Correct Result
#
# time=520000 Multiplicand= 8 Multiplier= 4 Product= 32 Done=1 Correct Result
#
# time=780000 Multiplicand= 7 Multiplier= 9 Product= 63 Done=1 Correct Result
#

```


- The waveforms shown are of 3 views: the overall waveform, a zoomed in section to show the correct results from input pairs, and the transcript to demonstrate that each case yielded the correct result
- The multiplier behaves correctly because upon loading two numbers to be multiplied, and by setting start to high, this starts the internal cycle of states, and once the final product has been calculated, it is outputted with the done signal going high
- Then upon the next clock cycle, product resets to 0, and the multiplier idles until a new pair of numbers is loaded along with the pull up of the start input

# Booth Multiplier

## Code

```
1 timescale 1ns/1ps
2 //include "carry_lookahead_adder.sv"
3
4 module booth_multiplier // Module start declaration
5 #(parameter N=4) // Parameter declaration
6
7 (
8     input clock, reset, start,
9     input logic signed [N-1:0] multiplicand, multiplier,
10    output logic signed [(2*N)-1:0] product,
11    output logic done
12 );
13
14 //Variable to store 2's complement of Multiplicand
15 logic [N:0] multiplicand_neg;
16
17 // Count variable for ADD/SHIFT stages
18 logic [$clog2(N)-1:0] count;
19
20 // Register to store Adder sum and multiplier
21 logic signed [(2*N)+1:0] shift_reg;
22
23 // Register to load multiplicand value
24 logic signed [N:0] load_reg_pos;
25 logic signed [N:0] load_reg_neg;
26
27 // wires to connect with carry lookahead adder
28 logic [N:0] add_operand1, add_operand2;
29 logic c1a_carry;
30
31 // next_state encoding and next_state variable
32 enum logic [2:0] {
33     IDLE = 3'b000,
34     INITIALIZE = 3'b001,
35     TEST = 3'b010,
36     ADD = 3'b011,
37     SHIFT_AND_COUNT = 3'b100,
38     DONE = 3'b101
39 } next_state;
40
41 // Instantiate (N+1)-bit carry lookahead adder
42 //Use add_operand1, add_operand2, sum to connect carry lookahead adder
43 //Hint: Carry out from the adder is ignored in our calculations and output sum
44 //has same length as add_operand1 and add_operand2
45 // Tie CIN to '0'
46 carry_lookahead_adder #(N(N+1)) adder_inst(
47     .A(add_operand1),
48     .B(add_operand2),
49     .CIN(1'b0),
50     .result(sum)
51 );
52
53 // Create negative multiplicand value
54 assign multiplicand_neg = ~multiplicand;
55
56 always_ff@(posedge clock, posedge reset) begin
57     if(reset) begin
58         count <= 0;
59         next_state <= IDLE;
60         load_reg_pos <= 0;
61         load_reg_neg <= 0;
62         shift_reg <= 0;
63     end
64
65     else begin
66         case(next_state)
67             IDLE: begin
68                 if(!start) begin
69                     next_state <= IDLE;
70                 end
71                 else begin
72                     next_state <= INITIALIZE;
73                 end
74             end
75             INITIALIZE: begin
76                 load_reg_pos <= multiplicand;
77                 load_reg_neg <= multiplicand_neg[N:0];
78                 shift_reg <= {1'b0, {N{1'b0}}}, multiplier, 1'b0;
79                 next_state <= TEST;
80                 count <= 0;
81             end
82             TEST: begin
83                 if(shift_reg[1:0] == 2'b01) begin
84                     next_state <= ADD;
85                     add_operand1 <= load_reg_pos;
86                     add_operand2 <= shift_reg[(2*N)+1:(2*N)-3];
87                 end
88                 else if(shift_reg[1:0] == 2'b10) begin
89                     next_state <= ADD;
90                     add_operand1 <= load_reg_neg;
91                     add_operand2 <= shift_reg[(2*N)+1:(2*N)-3];
92                 end
93                 else begin
94                     next_state <= SHIFT_AND_COUNT;
95                     add_operand1 <= {sum, shift_reg[N:0]};
96                 end
97             end
98             ADD: begin
99                 next_state <= SHIFT_AND_COUNT;
100                 shift_reg <= {sum, shift_reg[N:0]};
101             end
102             SHIFT_AND_COUNT: begin
103                 shift_reg <= (shift_reg >> 1); // Right Arithmetic shift e
104                 if(count == N-1) begin // If 'N' times SHIFT operation perf
105                     next_state <= DONE;
106                 end
107                 else begin
108                     next_state <= TEST;
109                     count <= count + 1;
110                 end
111             end
112         endcase
113     end
114
115     done = (next_state == DONE) ? 1 : 0;
116     assign product = (next_state == DONE) ? {shift_reg[(2*N)], shift_reg[(2*N):1]} : 0;
117 endmodule: booth_multiplier
```


RTL netlist

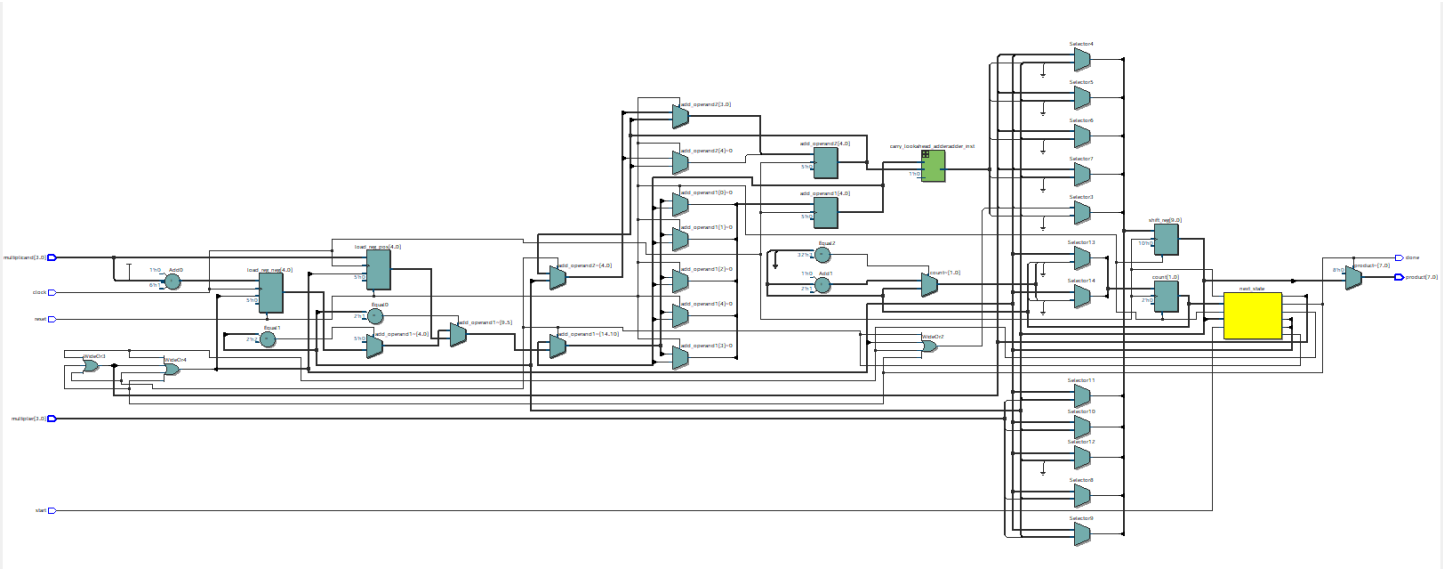

Resource usage



	Resource	Usage
1	Estimated ALUTs Used	43
1	-- Combinational ALUTs	43
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	36
3		
4	Estimated ALUTs Unavailable	1
1	-- Due to unpartnered combinational logic	1
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	43
7	Combinational ALUT usage by number of inputs	
1	-- 7 input functions	1
2	-- 6 input functions	3
3	-- 5 input functions	2
4	-- 4 input functions	13
5	-- <=3 input functions	24
8		
9	Combinational ALUTs by mode	
1	-- normal mode	42
2	-- extended LUT mode	1
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	49
12		
13	Total registers	36
1	-- Dedicated logic registers	36
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	20
17		
18	DSP block 18-bit elements	0
19		

## State diagram

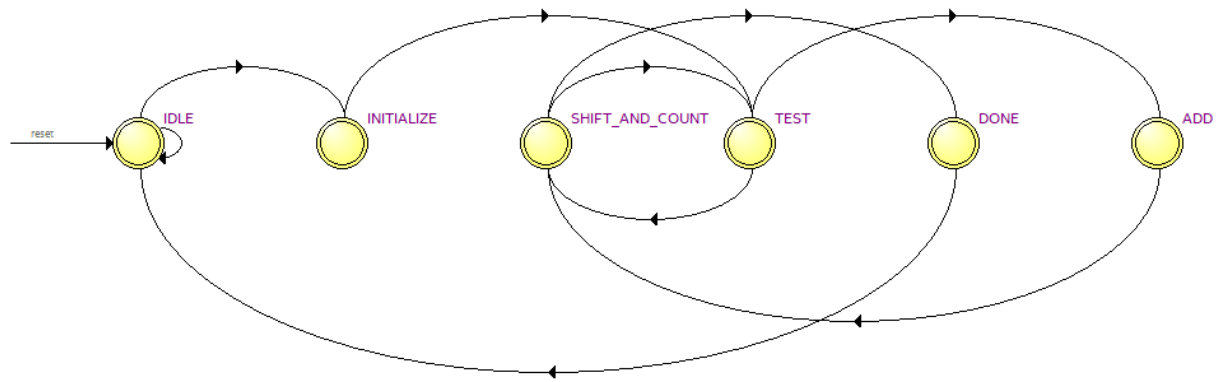

	Source State	Destination State	Condition
1	ADD	SHIFT_AND_COUNT	
2	DONE	IDLE	
3	IDLE	INITIALIZE	(start)
4	IDLE	IDLE	(!start)
5	INITIALIZE	TEST	
6	SHIFT_AND_COUNT	TEST	(!count[0]) + (count[0]).(!count[1])
7	SHIFT_AND_COUNT	DONE	(count[0]).(count[1])
8	TEST	SHIFT_AND_COUNT	(!shift_reg[0]).(!shift_reg[1]) + (shift_reg[0]).(shift_reg[1])
9	TEST	ADD	(!shift_reg[0]).(shift_reg[1]) + (shift_reg[0]).(!shift_reg[1])

## Testbench simulation waveform

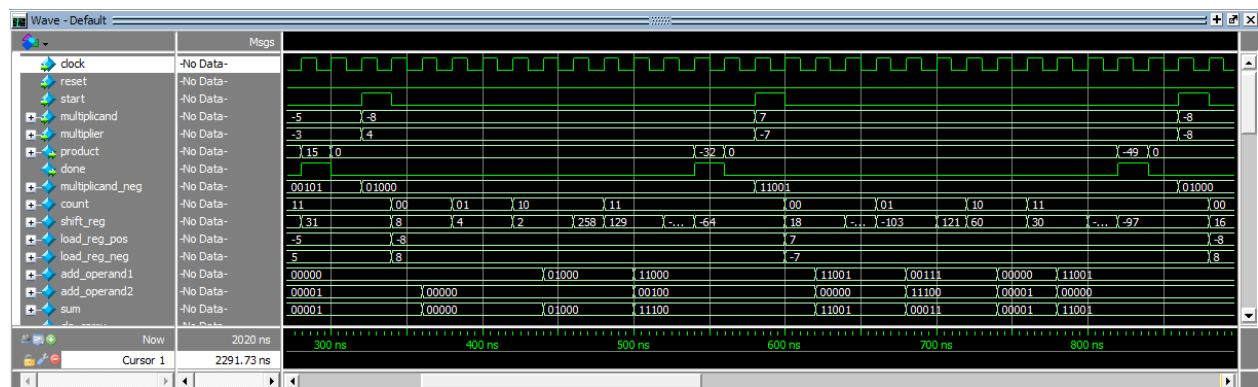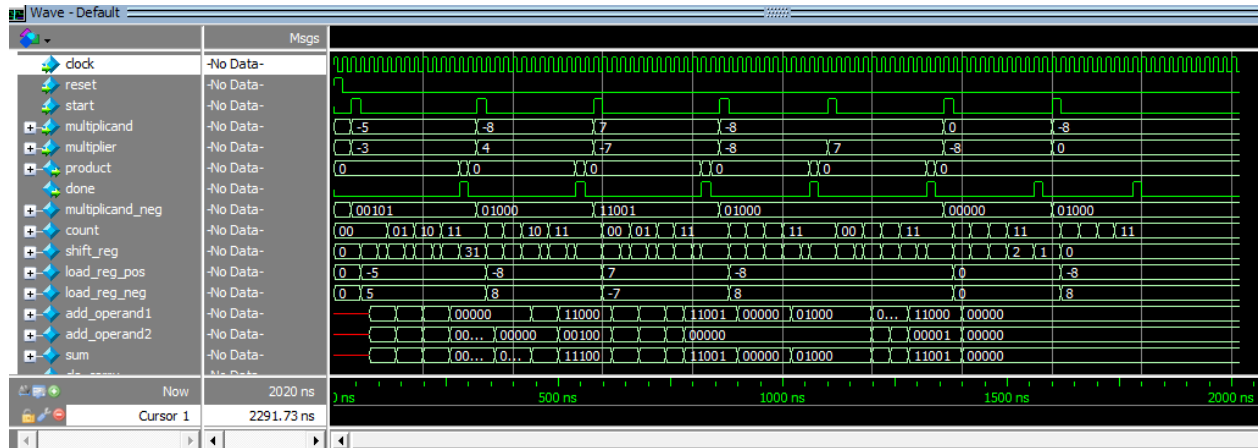

```

VSIM 8> run -all
# time=280000 Multiplicand= -5 Multiplier= -3 Product= 15 Done=1 Correct Result
#
# time=540000 Multiplicand= -8 Multiplier= 4 Product= -32 Done=1 Correct Result
#
# time=820000 Multiplicand= 7 Multiplier= -7 Product= -49 Done=1 Correct Result
#
# time=1060000 Multiplicand= -8 Multiplier= -8 Product= 64 Done=1 Correct Result
#
# time=1320000 Multiplicand= -8 Multiplier= 7 Product= -56 Done=1 Correct Result
#
# time=1560000 Multiplicand= 0 Multiplier= -8 Product= 0 Done=1 Correct Result
#
# time=1780000 Multiplicand= -8 Multiplier= 0 Product= 0 Done=1 Correct Result
#
A ** Note: $finish : C:/Banco/EECE 111/HW5/Tab5/booth_multiplier/booth_multiplier_testbench

```



- The waveforms shown are of 3 views: the overall waveform, the zoomed in waveform to show 3 cases and their outputs, and the transcript to demonstrate that each case yielded the correct result
- The multiplier behaves correctly because upon loading two numbers to be multiplied, and by setting start to high, this starts the internal cycle of states, and once the final product has been calculated, it is outputted with the done signal going high
- Then upon the next clock cycle, product resets to 0, and the multiplier idles until a new pair of numbers is loaded along with the pull up of the start input